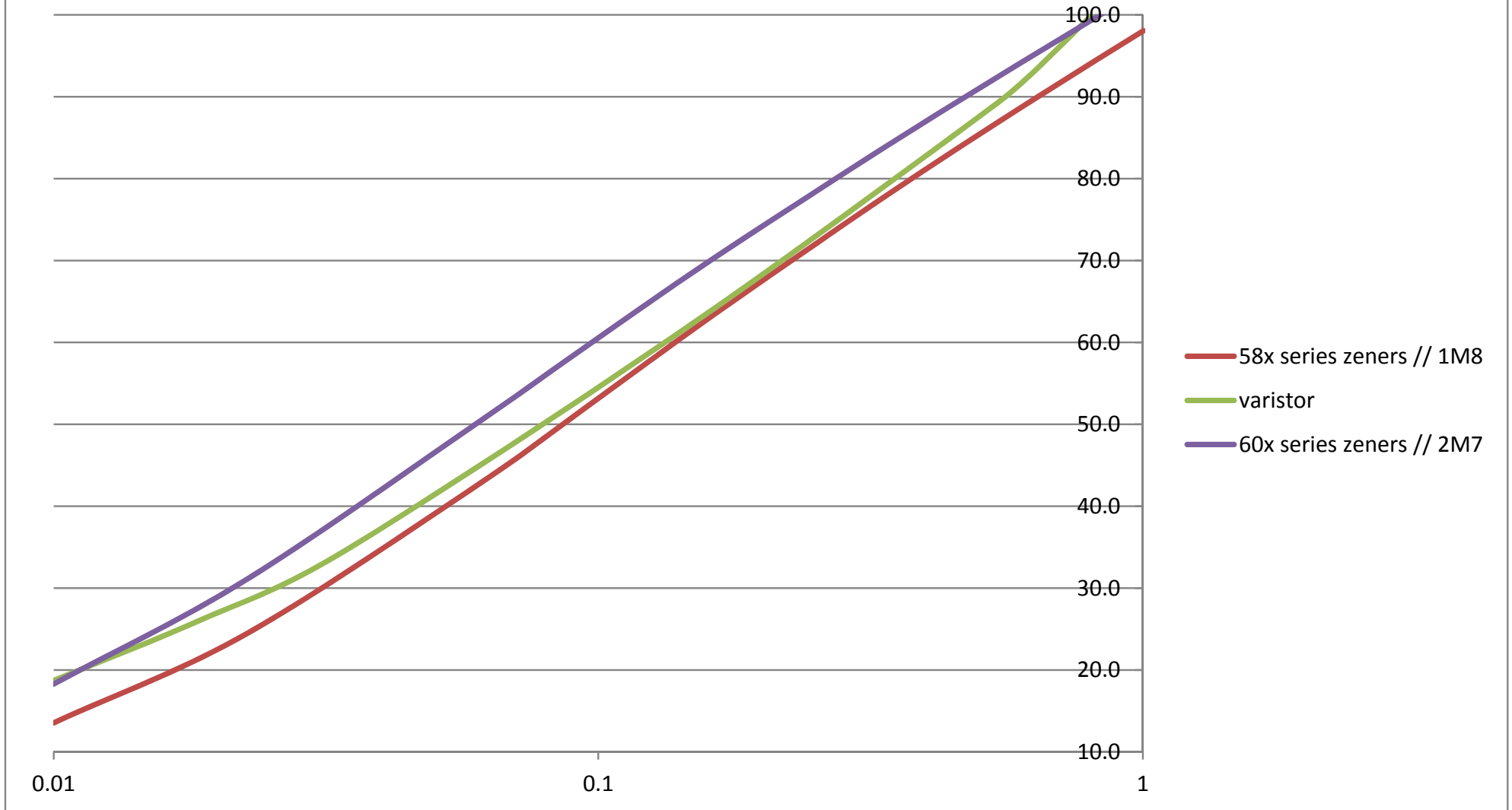
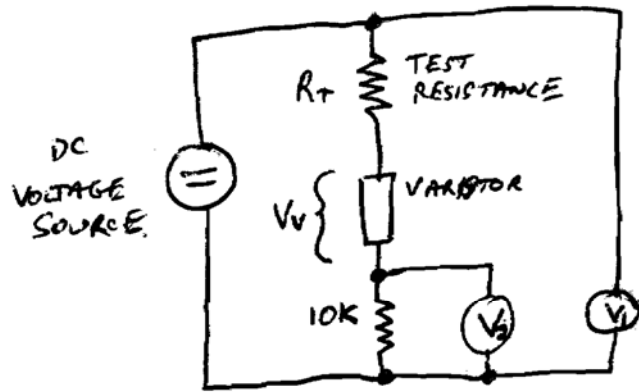


## Varistor voltage vs current (V,mA) series 3V3 zeners with shunt resistor



### Magnatone varistor measurement info

243VDC supply with a range of test resistors from 220kΩ to 24MΩ.  
 Meter for V2 with 10MΩ input resistance. All test resistances and voltages within about 1% tolerance.



$$V_v = V_1 - (R_T + 10k) \cdot \frac{V_2}{10k}$$

$$I_v = \frac{V_2}{10k}$$

Varistor 1

RT (kΩ)	Iv (mA)	Vv (V)	kohm
24000	0.0104	23.3	2240
12000	0.0202	30.4	1505
6000	0.0388	39.8	1026
3410	0.0653	49.7	761
1520	0.1374	62.8	457
1015	0.198	70.1	354
694	0.277	77.0	278
400	0.447	88.8	199
219	0.742	101.1	136

Varistor 2

RT (kΩ)	Iv (mA)	Vv (V)	kohm
24000	0.0103	26.7	2592
12000	0.02	33.8	1690
6000	0.0384	43.2	1125
3410	0.0646	53.1	822
1520	0.136	64.9	477
1015	0.196	72.1	368
694	0.2745	79.8	291
400	0.443	90.4	204
219	0.737	102.3	139

Cloned varistor: 36 x 3V6 zeners in series. 2M2Ω in parallel with 32x zeners. 220kΩ in parallel with 15x zeners. 47kΩ in parallel with 6x zeners	RT (kΩ)	Iv (mA)	Vv (V)	kohm
	24000	0.0103	26.7	2592
	12000	0.02	33.8	1690
	6000	0.0385	42.6	1107
	3410	0.0646	53.1	822
	1520	0.136	64.9	477
	1015	0.197	71.1	361
	694	0.276	78.7	285
	400	0.444	90.0	203
	219	0.747	100.0	134

# Varistor voltage vs current (V,mA)

Clone = 36x 3V6 in series: 2M2@32; 220k@15; 47k@6 shunt resistors

