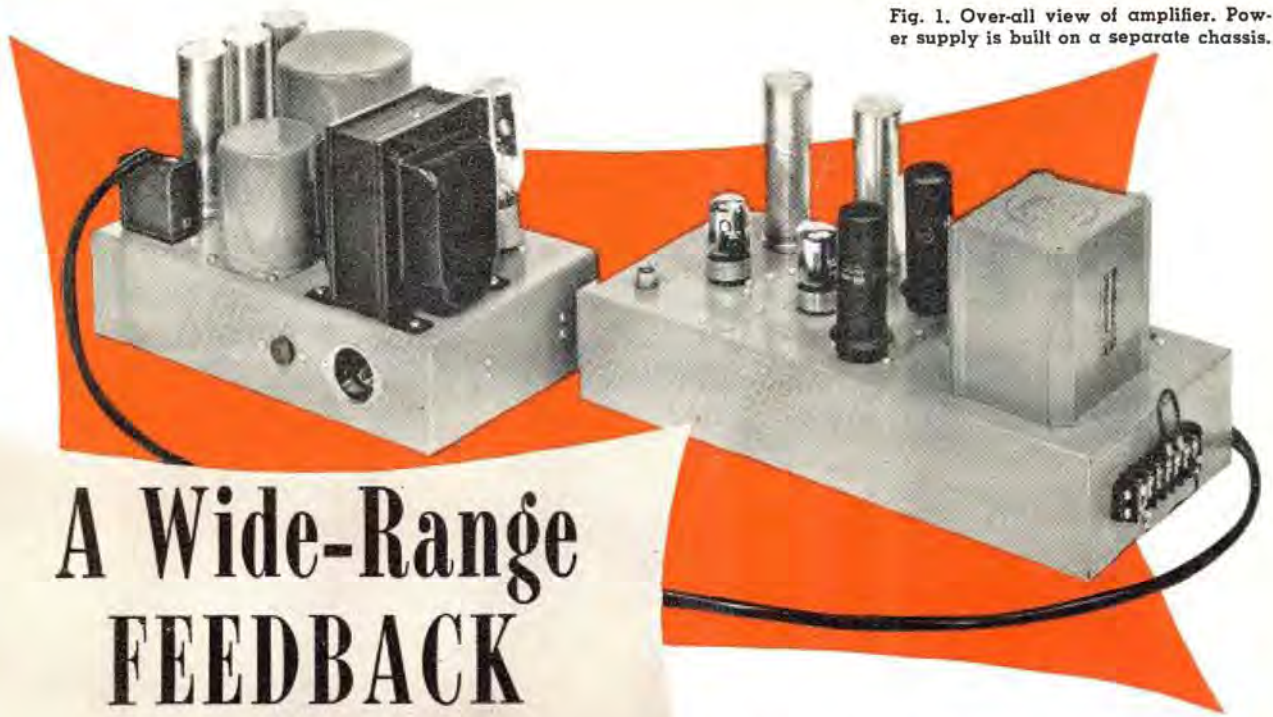


Fig. 1. Over-all view of amplifier. Power supply is built on a separate chassis.



# A Wide-Range FEEDBACK AMPLIFIER

*Inverse feedback over 4 stages proved no problem to author in designing this American version of the "Williamson Amplifier."*

By

**ROBERT M. MITCHELL**

Circuit Application Engineer, United Transformer Co.

**T**HE growing demand for increased realism in the reproduction of sound, both in music and speech, has necessitated a reconsideration of several basic problems in the design of audio amplification equipment. These problems are concerned with psychological as well as physical phenomena, and involve such varied considerations as system bandwidth, room acoustics, the sensation of loudness, and the relationship between dis-


tortion products and musical dissonance, to name only a few. In this continued striving for more faithful reproduction, negative feedback plays an indispensable part.

At one time negative feedback was used somewhat as a remedy, that is, it ameliorated gross defects in equipment of mediocre quality until some of the resultant specifications were comparable to those of higher quality equipment. Fortunately for the music-

lover, those days are largely past, and feedback is now more profitably employed in refining the characteristics of an already superior system. Thus, it is becoming more common to find large amounts of feedback being used with medium-power, all-triode amplifiers of very linear characteristics, employing parts of the highest quality. The employment of such large amounts of feedback requires that, for stability's sake alone, the gain-frequency and phase-frequency characteristics of the original amplifier be controlled over a range much greater than that over which the benefits of the feedback are desired. Terman, in his "Radio Engineers Handbook," page 226, gives as an approximate rule the relation of one octave extension of range for every 10 db. of feedback desired, plus one or two octaves as a margin of safety. Thus, if it is desired to produce an amplifier with 20 db. of feedback and a useful range of 20 to 20,000 cycles, it is necessary that the characteristics of the feedback loop be controlled for at least three octaves beyond this range, or from 2.5 cycles to 160,000 cycles. Since the control of gain characteristics is a comparatively simple matter for resistive-capacitive coupled stages, the crucial component in a high-quality amplifier is the output transformer.

A high-quality amplifier of excellent linearity and utilizing 20 db. of feedback around all four stages and the output transformer has recently

Fig. 2. Schematic diagram and parts list covering the amplifier power supply.

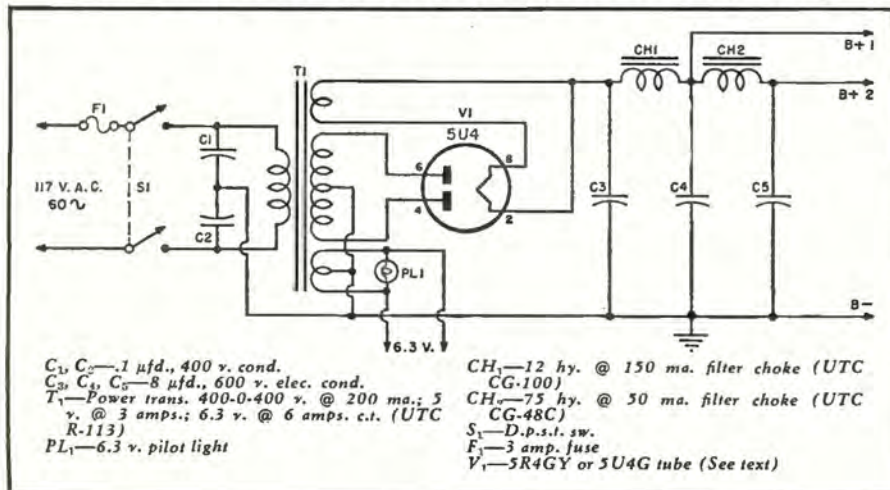

been developed in England by Mr. D. T. N. Williamson. This "Williamson" amplifier was literally designed around a special output transformer, and used standard English parts. It is the purpose of this article to describe an outstanding version of this amplifier which uses a stock output transformer and standard American parts.

The heart of the amplifier is the output transformer, UTC LS-63. This transformer matches push-pull loads of 10,000 and 6000 ohms to a wide range of voice coil impedances. The frequency response of the transformer alone extends smoothly within 1 db. from 15 cycles to 50 kc. at medium power levels. This response enables the entire amplifier to be incorporated in the feedback loop with complete freedom from instability. The resulting feedback amplifier has a frequency characteristic which is flat within 1 db. from 10 cycles to 100 kc.!

The amplifier circuit is straightforward and simple. As may be seen from Fig. 3, it consists of four stages; a voltage amplifier, direct-coupled to a split-load phase inverter, a push-pull voltage amplifier, and a push-pull power amplifier stage. The output tubes are 1614's, connected as triodes, with self bias. Except for a lower maximum plate voltage rating, this tube is electrically identical to the 807, but has the additional advantages of being single-ended in construction and having a standard octal base.

In order to permit flexibility of operation, the amplifier was built on two chassis, one containing the amplifier proper, and the other the power supply. Figs. 1 and 5 show the top-chassis and under-chassis views respectively of the two units. Point-to-point wiring is used throughout, with short, rigid leads and a common ground bus serving to reduce stray coupling and hum pickup. The ground bus picks up the individual grounds in order, starting at the highest level stages and progressing in order to the lower stages, where it is finally grounded to the chassis at the input.

The performance of the amplifier depends to a large extent on the balance of the push-pull stages. The output transformer constants (inductance, leakage, etc.) are precision-balanced, so that no adjustments are needed for that component. The plate load resistors for the push-pull driver stage should be matched, as should also the plate and cathode resistors in the phase inverter stage. Before the amplifier is placed in operation, two simple adjustments must be made. These adjustments set the operating conditions for the output stage, and normally need be made only once.

Since the total plate dissipation for the two 1614's is 50 watts, the total cathode current must be limited to 120 milliamperes. This is accomplished by inserting a milliammeter in the common leg and adjusting  $R_{15}$ . This will produce a bias of about 38 volts when the plate to ground voltage is 440 volts, and will keep the static plate

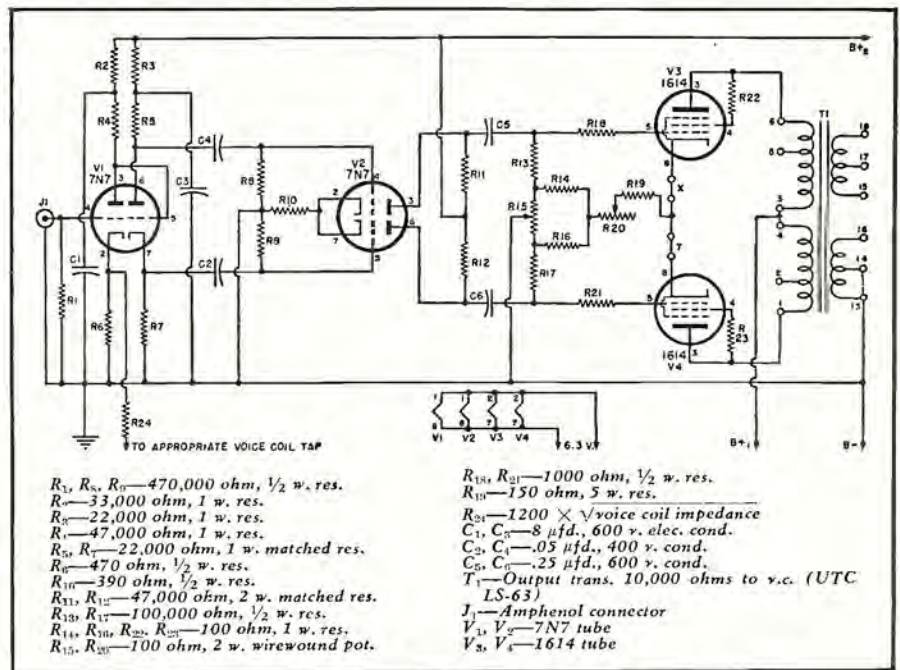


Fig. 3. Complete schematic diagram of the wide-range feedback amplifier unit.

dissipation within the 50 watt rating. After this is done, the standing currents in each tube are adjusted to equality by placing millimeters at points X and Y, and adjusting  $R_{15}$ . This adjustment reduces the unbalanced d.c. current in the output transformer primary, and, consequently, improves the low frequency response.

When adjusted according to the above instructions, the amplifier is operating almost completely in Class A, and will deliver 8 watts of power with almost undetectable distortion (less than 0.1%). Although this may seem to be a rather low power output, it is more than adequate for home listening. For reproduced music to sound at


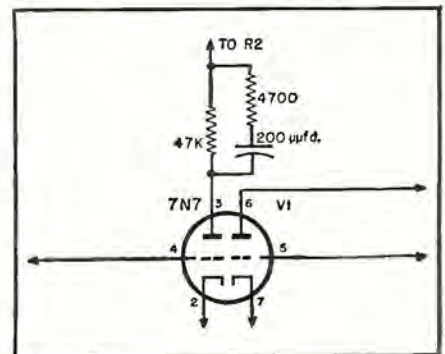


Fig. 4. Phase correcting network which can be used to eliminate the effects of excessive stray capacity or capacitive loads.

Fig. 5. Under chassis views of the audio amplifier and accompanying power supply.

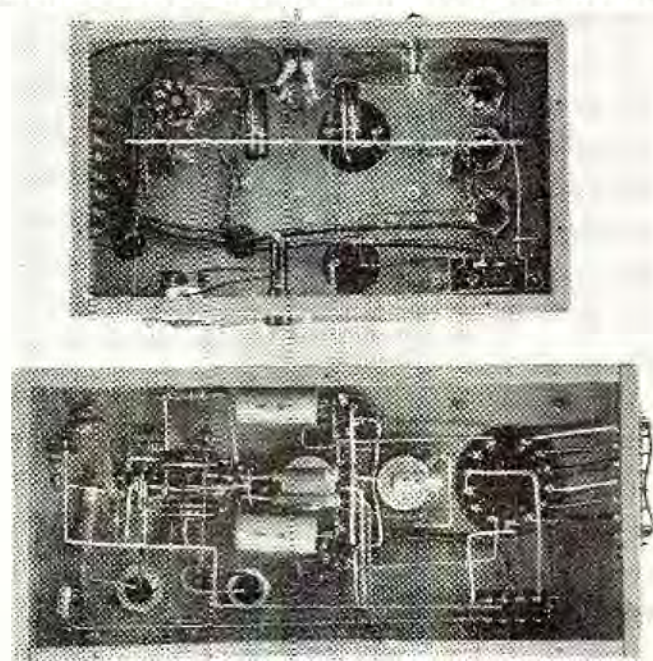

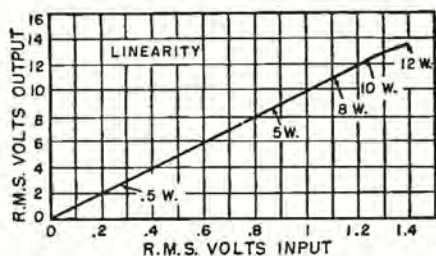


Fig. 6. Linearity curve of the amplifier.

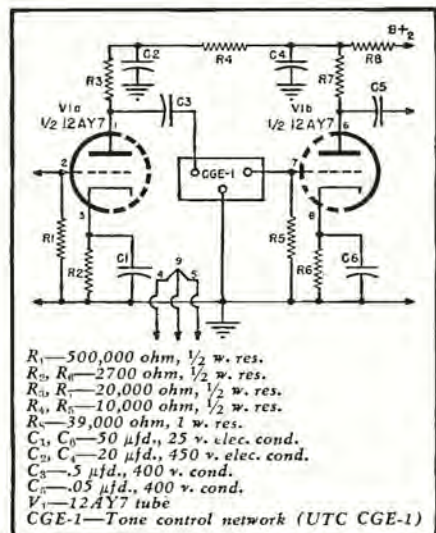


Fig. 7. An equalizing circuit, giving up to 15 db. boost or cut at either end of the spectrum, which may be used with amplifier.


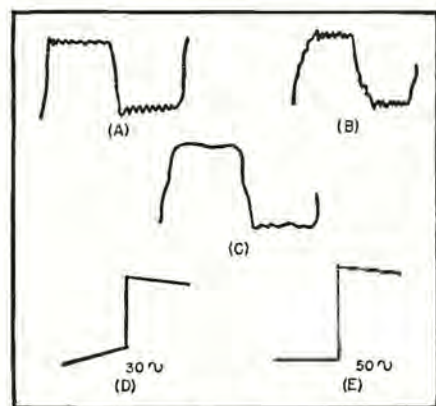


Fig. 8. Frequency response of the amplifier. See text for an explanation of waveforms.

Fig. 9. (A) Frequency response at different output levels for Class A operation, and (B) the frequency response of the amplifier in Class AB<sub>1</sub> operation at higher levels.

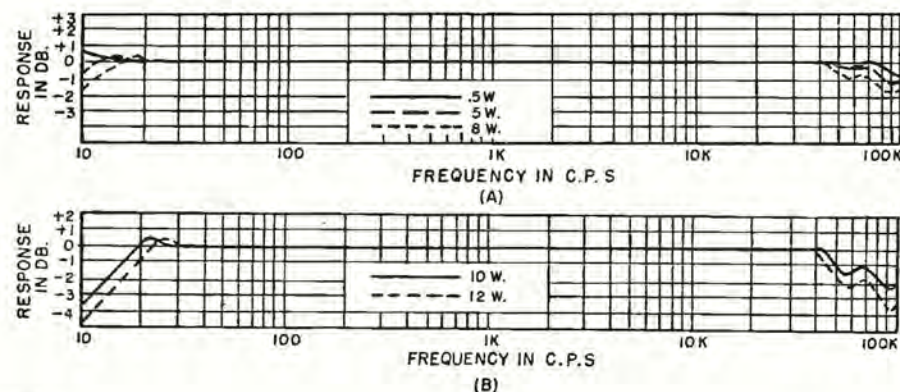

(Continued on page 166)

about concert level to the listener in a large-sized living-room requires an average of about 5 milliwatts of acoustic power. In a fair-sized living-room of say, 2500 cubic feet volume, a value half this great is adequate. Allowing an average of 20 db. (100 times as much power) for peaks, a value of 0.25 watts is obtained. To produce this acoustic power through a speaker system of 10% efficiency requires an electrical power of 2.5 watts. Under these conditions the 8 watt amplifier has a safety margin of undistorted power of more than 3 times, or 5 db. If more power is required, the bias may be changed so as to operate the output stage more in Class AB<sub>1</sub>, by adjusting  $R_{20}$  for 110 ma. total current (approximately — 40 volts bias), and adjusting  $R_{15}$  for equal currents as before. Under these conditions the distortion is 0.3% at 10 watts and 1% at 12 watts.

In the English design, a phase correcting network across  $R_1$  is a permanent part of the amplifier. This tends to increase the margin of stability at high frequencies. The leakage inductance of the UTC LS-63 is so low that this network is ordinarily not required. However, if the secondary load is highly capacitive or other stray capacities are introduced in the amplifier, it may be desirable to add this network. If the output tube currents are high when all components are properly connected and all other measurements are correct, it is usually an indication that the circuit is oscillating at a very high frequency due to the stray capacities mentioned above. In such cases, the phase correcting network shown in Fig. 4 will eliminate this.

The power provided by the power transformer and that dissipated by the output tubes in particular is considerably larger than in most home amplifiers. Consequently, the constructor must allow for adequate ventilation when mounting the unit in cabinets, etc.

If the "B<sub>+</sub>" voltage is too high, because of high line voltage, for example, the 5R4GY tube (Fig. 2) should be used in place of the 5U4G. This tube may be plugged directly in the same socket, since the basing is iden-

tical, and due to its larger internal drop, will give a lower output voltage.

The performance characteristics of this amplifier are illustrated in tabular and graphic form in Figs. 6, 8, and 9. All of the measurements were made with a source resistance of 50,000 ohms and a non-inductive resistor of 15 ohms connected to the 15 ohm secondary terminals of the output transformer.

Fig. 9A shows the frequency response at different output levels for Class A operation, while Fig. 9B shows the response for Class AB<sub>1</sub> operation at higher levels. The response of the amplifier with 40 volts bias is essentially the same at low levels as that of Fig. 9A. The linearity of the amplifier over the entire power range is shown in Fig. 6.

The low distortion content of this amplifier is outstanding. At 8 watts (actual measured power dissipated in the load resistor, not an "equivalent power") the distortion is less than one-tenth of one per-cent. Because the distortion is so minute, it is necessary that several precautions be taken in measuring it, in order to insure that spurious voltages such as noise, hum, etc. are not included in the results. The author has found that a satisfactory procedure is to pass the audio generator output through a low-pass filter of at least 60 db. attenuation and measure the harmonic components of the amplifier output with a wave analyzer.

One of the desirable features of audio amplifiers is low output impedance, and in this respect a negative feedback amplifier is unsurpassed. The ratio of the load resistance to the effective output impedance is called the damping factor, since it determines the effectiveness of the amplifier in damping vibrations originating in the loudspeaker.

A common value of damping factor for beam tubes with feedback or triodes without feedback is 3. The damping factor of this amplifier is 27, equivalent to an output impedance of 0.55 ohm at the 15 ohm secondary. This ability of the amplifier to damp the loudspeaker contributes substantially to the "cleanness" of reproduction.

Another factor contributing to clarity in reproduction is the transient response. Because of the ease of interpretation involved, transient response is usually tested by means of square waves. The high frequency square wave response of the amplifier is shown in Fig. 8. In this diagram (A) represents the response of the entire amplifier to a square wave of 10 kc. repetition rate. The rapidity with which the maximum value is attained, i.e., the short rise time, is a graphic indication of the extremely small leakage inductance and stray capacitance of the output transformer. For comparison purposes the high frequency square wave response of a poorly designed unit is shown in Fig. 8B.

# ELECTRONICS TECHNICIANS

FOR

## RADAR, COMMUNICATIONS, TELEVISION RECEIVERS

Needed By

RCA SERVICE COMPANY, INC.

A Radio Corporation of America Subsidiary

For U. S. and Overseas

### REQUIREMENTS:

- Good Character
  - Training in Installation or Maintenance of Radar, Communications or Television
  - Give Full Details of Practical Experience
- Qualified candidates will be interviewed Promptly.

Qualified technicians seeking connection with leading company having permanent program for installation and service of military equipment, AM, FM, TV transmitters and receivers, and electronic devices, such as electron microscopes, mobile and microwave communications, theatre TV, write full history to:

**RCA SERVICE COMPANY, INC.**  
CAMDEN 2, NEW JERSEY

### COMPENSATION:

Up to \$7,000.00 a year to start For Overseas Assignment With Periodic Review of Base Salary Thereafter Made up of—

- Base Salary
- Overseas Bonus
- Actual Living and other Expenses
- Accident, Hospitalization, and Life Insurance
- Vacation and Holiday Pay

## RADAR, COMMUNICATIONS AND SONAR TECHNICIANS W-A-N-T-E-D For Overseas Assignments

### Technical Qualifications:

1. At least 3 years practical experience in installation and maintenance.
2. Navy veterans ETM 1/c or higher.
3. Army veterans TECH/SGT or higher.

### Personal Qualifications:

1. Age, over 22—must pass physical examination.
2. Ability to assume responsibility.
3. Must stand thorough character investigation.
4. Willing to go overseas for 1 year.

Base pay, Bonus, Living Allowance, Vacation add-up to \$7,000.00 per year. Permanent connection with company possible.

Apply by Writing to  
**D-4, P.O. Box 3575;**  
**Philadelphia 22, Pa.**

Men qualified in RADAR, COMMUNICATIONS or SONAR give complete history. Interview will be arranged for successful applicants.

## • VIDEO-VEND COIN OPERATED TELEVISION

Get in on the ground floor of this SENSATIONAL, PROFITABLE business. For small investment we can show you large returns. Requires only a few hours a week. Write—

Coin Radio & Television Corp.  
190A Duane St. Dept. R New York City

## GET THE LATEST IN RADIO & TELEVISION New 7-Volume Set FREE for 7 days trial

### APPLIED PRACTICAL RADIO-TELEVISION

with Television Servicing  
MAKE MORE MONEY  
Servicing the Tough  
Radio-Television Jobs

This new, 7-volume set gives you solid working knowledge of Radio and Television. Very latest on Television Servicing, UHF and Color TV. Everything from fundamentals to newest in FM, TV, Electronics, etc. Clear, practical! Tells you how to construct, install, service. Short-cut trouble-shooting methods. Handy "on the job" Radioman's Handbook included. More than 2500 pages, 1200 illustrations, charts, diagrams.

**FREE TRIAL OFFER:** Examine these great, pay-raising books for 7 days at our expense. Just mail coupon below.

**FREE RADIO-TELEVISION DIAGRAMS BOOK**  
Act at once and get new book of "150 Radio-Television Diagrams Explained." FREE for asking to see the 7-Book Set. You owe nothing if you send the set back at our expense in 7 days. If you keep the set, pay only \$3 in postage is paid, or \$22 cash now. Either way, book is yours! Send coupon TODAY! It's just a request to see Set and get Diagrams book Free. Act now!

### GOOD FOR FREE TRIAL and FREE BOOK!

Educational Book Publishing Division  
COYNE ELECTRICAL & RADIO SCHOOL  
500 S. Paulina St., Dept. AQ-73, Chicago 12, Ill.  
Rush 7-Volume "Applied Practical Radio-Television,"  
postpaid, for 7 days' FREE Trial per your offer. In-  
clude FREE Book of 150 Radio-Television Diagrams.  
Name..... Age.....  
Address.....  
Town..... Zone..... State.....

## Feedback Amplifier (Continued from page 68)

The curvature of the leading edge is an indication of poorer high frequency characteristics. The amplifier's response without feedback may also be seen in Fig. 8C. The small oscillations on the top of the square wave pattern are due to the shock excitation and are quite normal. They are of small amplitude and very high frequency, and have no effect on the amplifier performance in the audio range.


In making square wave tests it is essential that a wide range oscilloscope be used, since otherwise the waveform seen on the screen will be completely different from that entering the oscilloscope. Ordinary oscilloscopes are generally quite unsatisfactory for this purpose, since the required flat frequency range is at least from 10 cycles to 2 megacycles.

The low frequency square wave response is shown in Figs. 8D and E. The extremely slight tilt in the top of the wave is indicative of the large primary inductance (150-200 henrys) and small phase shift (12 windings interleaved) of the transformer.

The amplifier described was designed to be a power-amplifier unit of such optimum characteristics that improvements in other components in a complete system would never make the main amplifier the weak link in the chain. Consequently, there have been no provisions for control functions or frequency compensating equipment, since these could be more readily changed if they were physically separate from the main amplifier.

In order to make a complete unit

Fig. 10. Diagram of a commercial equalizer-amplifier for a variable reluctance pickup.

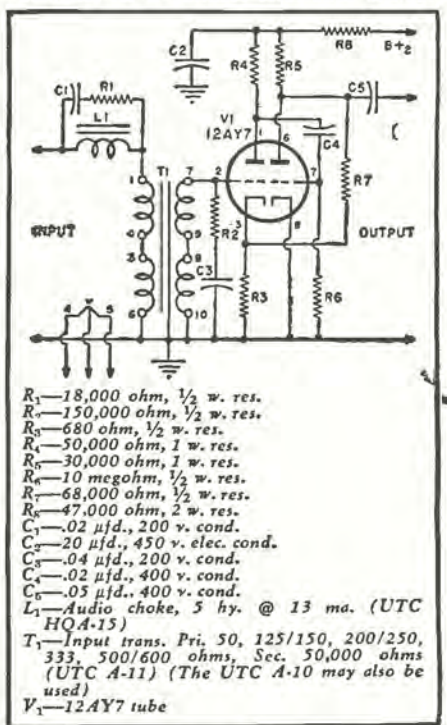

for highest-quality home listening, the following auxiliary equipment is desirable: 1. Volume Control, 2. Bass and treble equalization, 3. Reluctance-type pickup compensation.

The first control is readily achieved merely by making  $R_1$  a 500,000 ohm potentiometer. This is the only control which can be added to the body of the amplifier. Any additional tone controls or equalizing circuits must be placed before the amplifier, since if inserted internally, they would upset the feedback loop.

An excellent circuit giving up to 15 db. boost or cut at either end of the spectrum is shown in Fig. 7. When this circuit is used before the amplifier, the volume control should be  $R_1$  of the equalizer, in order to prevent overload of that circuit.

Fig. 10 shows a professional type equalizer-amplifier for the variable reluctance type pickup. This provides not only more accurate low frequency compensation, but also a slight high frequency roll-off to compensate for recording pre-emphasis.

Because it combines the desirable features of fidelity, simplicity, and economy, this amplifier is unusually attractive to the home builder. With this amplifier in his possession, the high fidelity enthusiast may be confident that he has a sound design that cannot be rendered obsolete by improvements in program material quality.

-30-

## TV IN BRAZIL

ON July 30 the Tupi television station at Rio de Janeiro, Brazil, transmitted the first of an announced series of four experimental public telecasts.

The show was broadcast from the studio of Radio Tamoio and viewed through receivers placed in the studio of Radio Tupi and at the entrances of the buildings housing the respective stations. The first broadcast was reported to be very successful and was enthusiastically received both by the studio audiences and the large crowds which gathered in the street.

Regular telecasting was scheduled to begin within thirty days of the original program, according to the U. S. Embassy report from Rio.

-30-





# Two Names You Can Depend Upon...



★ **RCA for Top Quality Equipment!**

★ **HUDSON for Best Value—Dependable Service!**

Our New Giant Store and Warehouse—3 Great Floors—features a Complete Line of RCA Equipment . . . Tubes, Batteries, Test Equipment and Parts . . . for Immediate Delivery or Shipment to All Parts of the World!

### RCA WV-97A SENIOR VOLTOHMYST

The WV-97A has a range of usefulness far beyond any other instrument in the field! Its quality, dependability, and accuracy make it ideal for TV in design laboratory, factory, and service shop. The Senior VoltOhmyst measures dc voltages in high impedance circuits, even with ac present. It reads rms value of sine waves and peak-to-peak values of complete waves or recurrent pulses, even in presence of dc. Its electronic ohmmeter has a range of 10 billion to one. Outstanding as a TV signal tracer. Includes direct probe and cable, dc probe, ohms lead, ground lead.

No. A14 .....Net **\$62.50**



### NEW! RCA 515S2 15" Duo-Cone SPEAKER

The newest development of Dr. H. F. Olson, RCA's renowned speaker authority. Delivers 25 watts of high fidelity audio over range of 40-12,000 cycles. Has two voice coils, each driving one of the duo-cones, which vibrate as a single cone, at crossover frequencies (around 2,000 cps), avoiding "crossover" interference. 2 lb. Alnico V magnet. Performance is amazing! 18 lbs.

No. A53, RCA 515S2 Speaker.....Net **\$48.50**  
RCA Model 515S1 15" Speaker, No. A52.....Net **\$35.57**

### RCA TELEVISION COMPONENTS

All RCA Television Components are "originals," designed with characteristics which are correct both electrically and mechanically for the tubes and circuits. They are "performance" proved and competitively priced!



### RCA INDUSTRIAL TUBES — Value Beyond Price!

RCA's unparalleled research facilities, engineering background, and manufacturing experience contribute to the quality, dependability, and operating economy of EVERY RCA tube you buy. The Quality of RCA tubes is Unquestioned!



### FREE! SEND FOR OUR NEW 1951 CATALOG

**HUDSON**  
RADIO & TELEVISION CORP.

212 FULTON STREET

NEW YORK 7, N. Y. • Digby 9-1192



Hudson Radio & Television Corp. Dept. 10R  
212 Fulton St., New York 7, N. Y.

Please send:  RCA WV-97A  515S2 Speaker  
 Full Payment Enclosed  
 Down Payment (10%)  
 SEND FREE HUDSON CATALOG—Just Out!

Name.....

Address.....

City.....Zone.....State.....

**Most Complete Stock of Radio, TV, Electronic and Sound Equipment in the East!**

### QUICK and EASY F.P. condenser replacement



New F.P.C. tool loosens old lugs, fastens new ones in a jiffy. Slim working end gets in past other parts. Long reach for deepest chassis. Can't slip. Lightweight, sturdy. Use it with one hand. Pays for itself on one tough job. Do not wait—order yours today. **only \$1.00** Postpaid in U.S.A. No stamps, please

K. D. Clayton, Box 1032, Bethlehem, Pa.

### Running Time Meters

Sangamo Model 17-B

In hours & 1/10th hours to 9999.9  
110/230 V, 60 cycles, A.C. (Please specify voltage.)

110/230 V.....\$4.50  
230 V only..... 3.50



### Variable Reset Timers

Sangamo Model 21

Opens circuit from 0 to 3 minutes, calibrated in 5 second intervals. Will handle 10 Amps or more (please specify voltage.)  
110/230 V....\$4.50 230 V only....\$3.50

FOB Oakland, 25% cash with order, balance COD.

**EMMONS RADIO SUPPLY**  
405 10th St. Oakland, Calif.