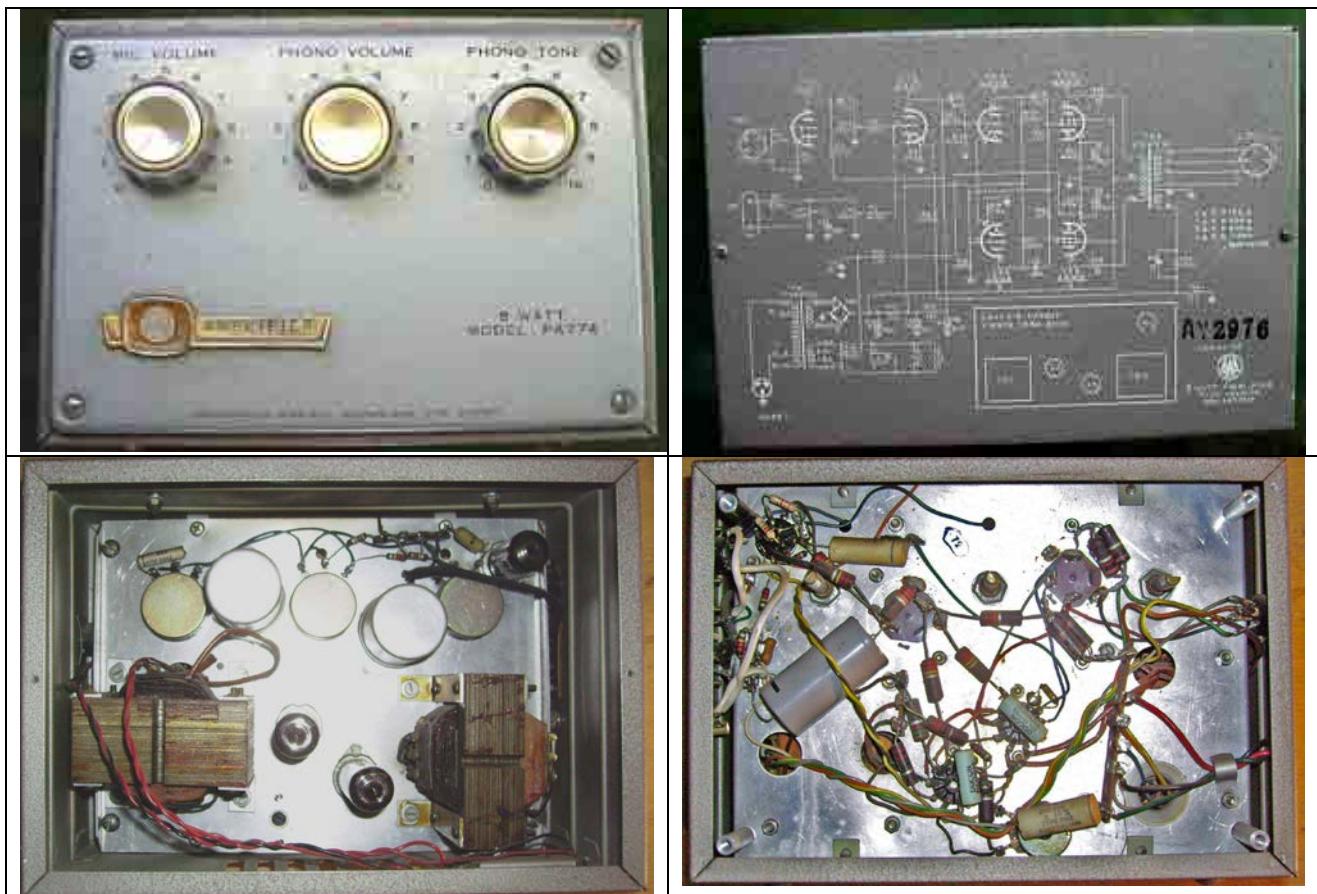


## 1. Summary

AWA 8 Watt Amplifier Type PA774, S.N. AY2976. eBay May 2009

### 1.1 Original design

One microphone and one P.U. input channel PA amplifier. Half 12AX7 amplifier for MIC channel. PU input summing into half 12AX7 summing amplifier. 6BM8 floating paraphrase splitter provides high gain to PP pentode output stage. Cathode bias push-pull 6BM8 output, with isolated secondary feedback winding taken to the 2<sup>nd</sup> stage cathode. 220V plate supply from FC442 bridge diode rectifier and capacitor filter. Plate supply fed direct to the screen supply. Cascading resistor/cap dropping to the splitter voltage supply, and again to the input amp supplies. 6.3VAC heater supplied to all valves, and hum cancelling feedback taken to cathode of V3B. Vol pot for MIC input. Vol pot for P.U. input. Tone pot for P.U. input. Output load settings 150/300/600/1200Ω from 5K PP transformer. Transformers marked with '60720' and '60195'. POTs are IRC marked with 59774T63 date codes suggesting 1963 manufacture. Modifications noted were: 2.5mm input jack added; 33uF 500V cap added across C9B. Problems included: Terminal strip cracked for AC termination. Cathode bias resistors degraded. Bridge rectifier MR1 (Westcode FC442) failed. C11A leaky. C9A,B high ESR.



### 1.2 Modified Design for Guitar Amp use

Inputs reduced to just one guitar input – isolated 6.5mm socket with tip grounded; changed R1 to 1M and 22K grid input added; R2 and R9 changed to 2K2; switched R9 bypass; R11 changed to 100K. PU circuitry and summer removed. Single tone pot with 1kHz notch at min end and treble roll off at max end using existing 500K pot with 180mH. 100nF & 1k series LCR on wiper to gnd, and with 2k2 and 560pF on wiper to top, with 22k from wiper to 0V. Inductor made from ferrite


common mode choke with windings in series (DCR=4Ω), and mu-metal outer shell screening (due to proximity of PT). Gain pot with 22pF treble bypass. Make-up stage with cathode boost switch.

Replaced AC cable. AC fuse added. AC input OFF (mid), Standby (down), ON (up) switch added - 100k bleed resistor across Standby switch to provide some positive bias of electrolytics before normal on state. Added new RS204 bridge rectifier and 120uF 400V cap for main filter. Yellow LED for standby using heater through 1N4148 and series 390R.


6.5mm phono locking socket for 15 ohm output, with switch to include 0R (up), 5R (down) or 10R (mid) series resistance (to match 5k transformer impedance) in series with 150R-to-300R output winding (ie. only using 15% of secondary 0-1200R winding). Removed orange and blue leads to power transformer primary. Removed other wiring taps on output transformer. Added 47k PRO2 across 0-1200R output winding of OPT to provide open-circuit loading ~0.2W dissipation at 8W output level. Added 330VDC MOVs across each OT primary half-winding.



330R screen stoppers and 15K grid stoppers added to output pentodes. C4, C6 lowered from 22nF to 10nF to minimise blocking distortion.

Phono Tone at min setting.

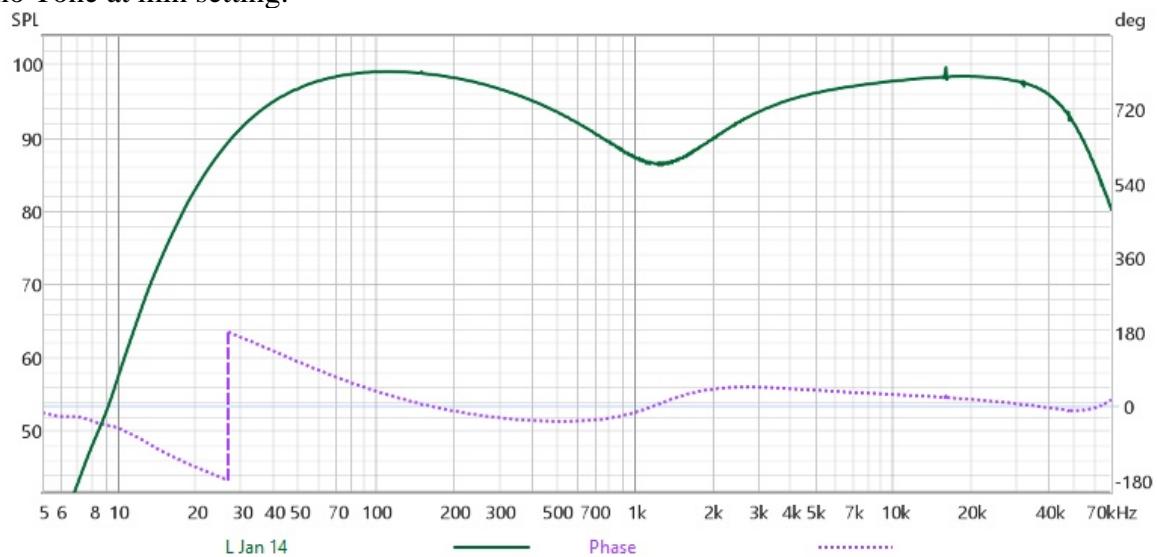

Phono Tone at 20% setting.

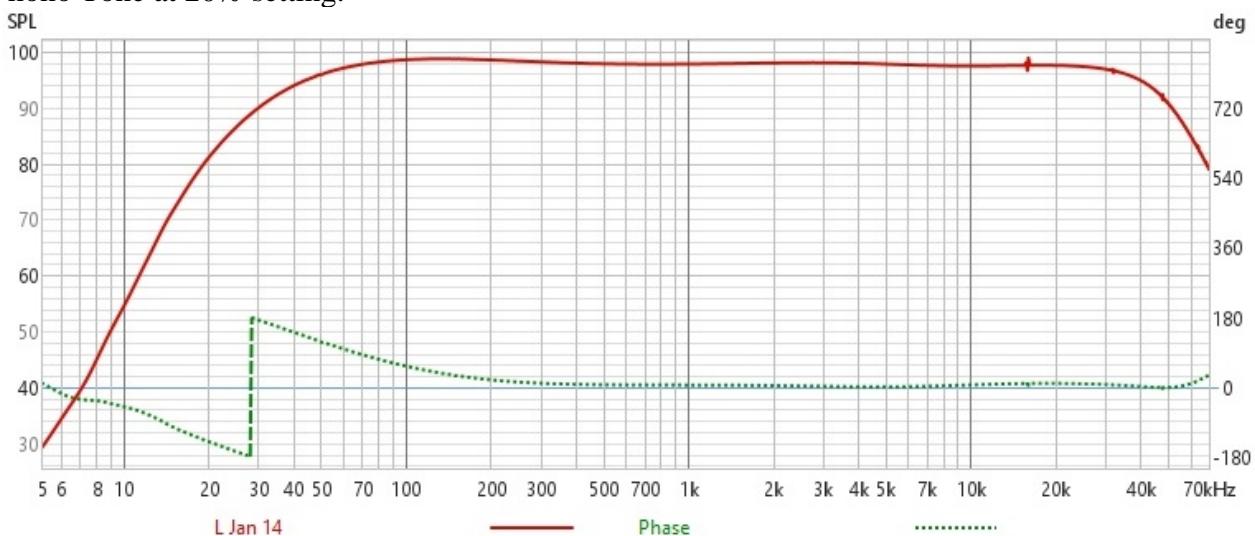

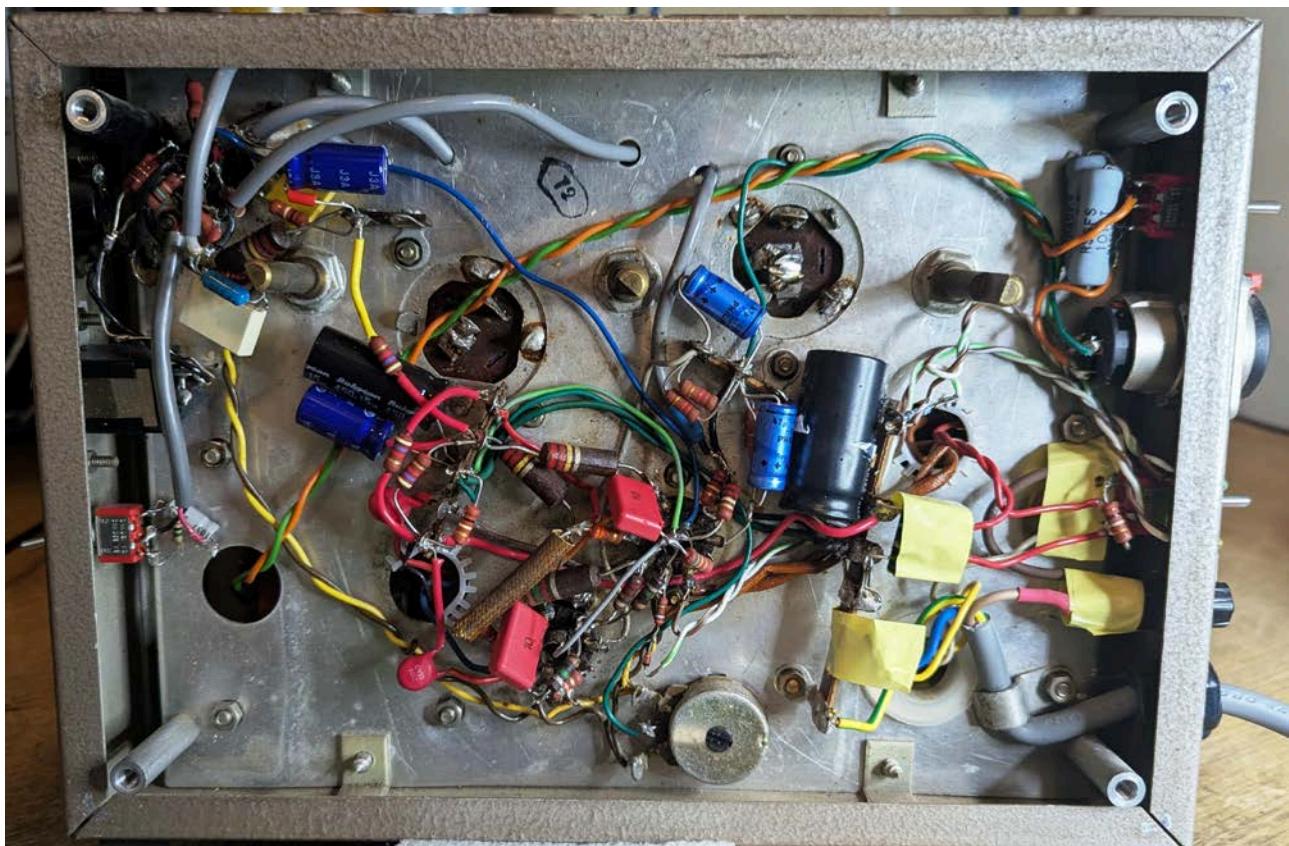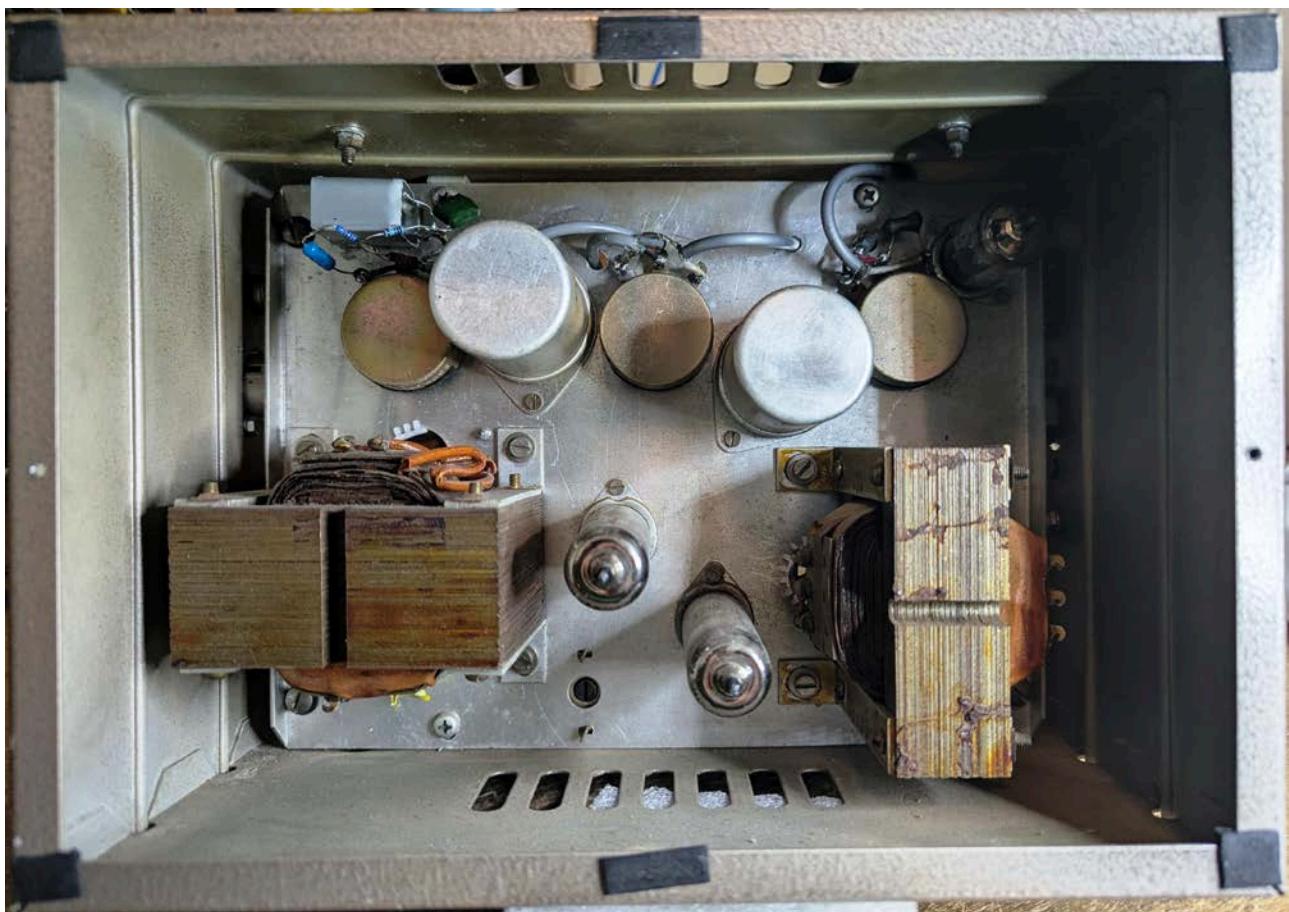

## 2. Measurements

Voltage rail regulation.

Rail	Idle	Cranked
VS1	244V (1.24Vrms)	
VS2	202V (30mVrms)	
VS3	233V	
VS4	227V	
Heater 1		
Sec HT		
Cathodes	18V, 18V (7W, 7W)	

Power transformer primary DC resistance: 59Ω.

Power transformer secondary DC resistance: 71Ω.

12VAC 50Hz nominal applied to output transformer 150R winding

Winding	Voltage rms	Turns ratio; Pri Impedance; Spec level; Notes;	turns %
Pri P-P: BLU to Vi	70.92	1 ; ; N/A; appears to be 5k P-P	
Sec: Feedback Winding	7.04	10.07; N/A; 49Ω, based on 5k P-P	20.2
Sec: 150 to Com	12.33	5.75; 4,960Ω; 150 Ω; based on 150	35.5
Sec: 300 to Com	17.43	4.07; 4,970Ω; 302Ω; based on 5k P-P	50.1
Sec: 1200 to Com	34.79	2.04; 4,994 Ω; 1201Ω; based on 5k P-P	100
Sec: 150 to 300	5.04	14.07; N/A; 25.2Ω; based on 5k P-P	14.5
Sec: 1200 to 300	17.28	4.1; N/A; 300Ω; based on 5k P-P	50

Output transformer primary DC resistance: 153Ω plate-to-plate.


Output transformer secondary DC resistance: 18.2Ω 1200 winding.

Output 6Wrms cranked into 17Ω.

### 3. Design Info

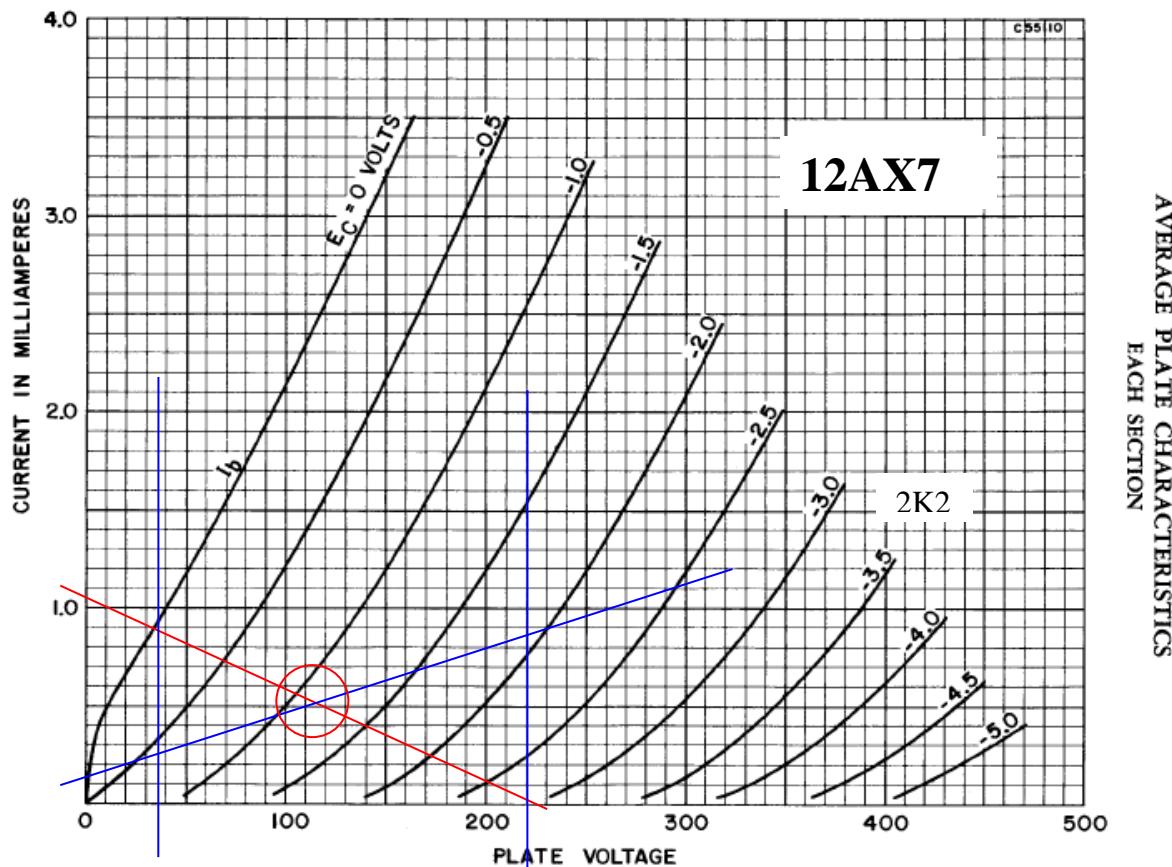
#### 3.1 Input stage – 12AX7 - modified

For the first half 12AX7, V1A: supply voltage  $VS4 = 227V$ ;  $V_a = V$ ;  $R_k = 2k2$ ;  $V_k = V$ ;  $I_a = mA$ ;  $R_{Ldc} = 220k$ . Second half is quite similar.


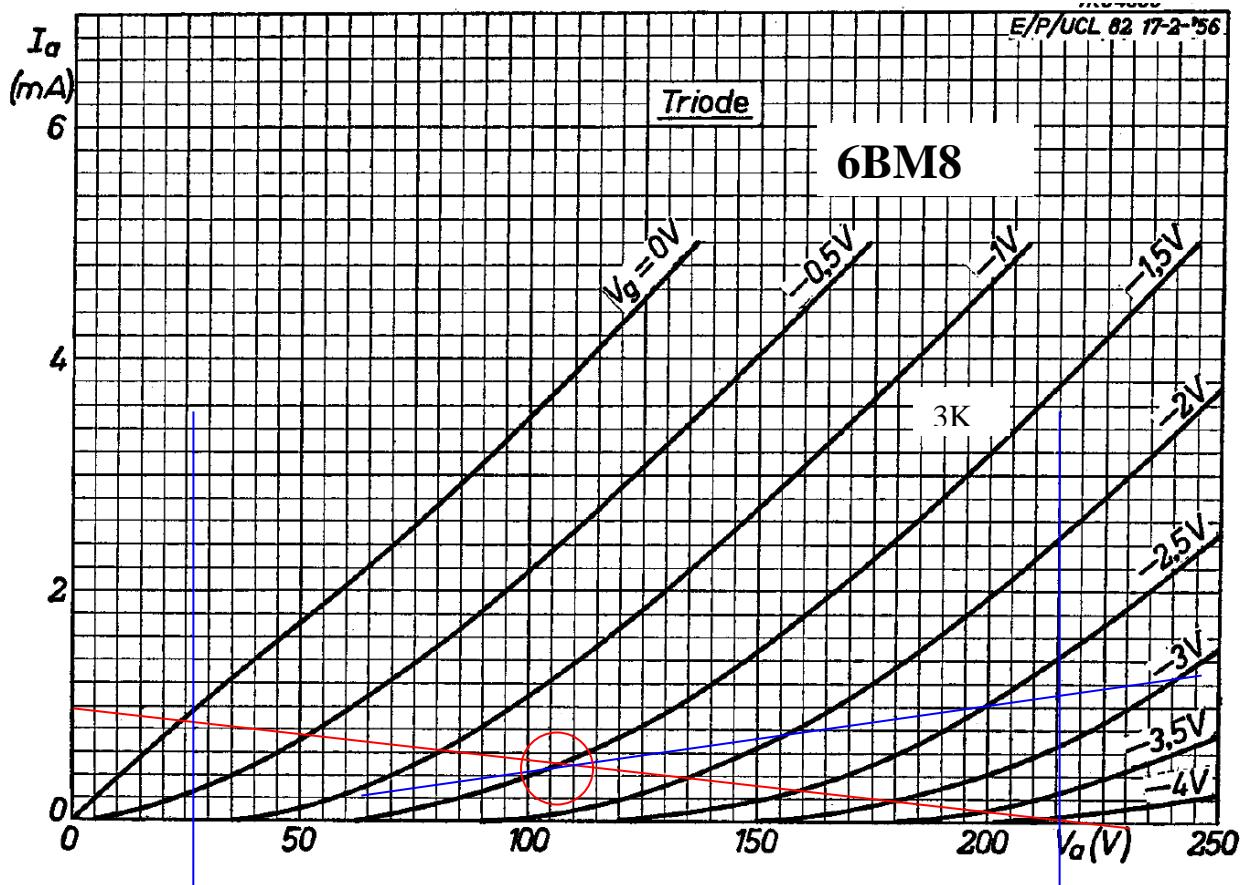
#### 3.2 Splitter stage – 6BM8 Triode

Cathode-coupled paraphase configuration phase splitter. Signal going into the grid of V2A makes a same-phase signal on the cathode and an opposite phase (and larger) signal on its plate. Triodes V2A and V3A share a common cathode resistor so when V2A is biased further into conduction, its increased cathode current raises the voltage of both cathodes so V3A is biased further out of conduction and so V3A plate signal varies with opposite phase of V2A plate voltage. If the voltage on plate of 'A' is larger than plate voltage of 'B' then grid of 'B' is driven harder, and so forces plate voltage of 'B' larger to equalise.



### 3.3 Output Stage

In this Class AB push-pull output stage, one tube is pushed into conduction and the other tube is pulled into cutoff, and there is a region of overlap where both tubes conduct equivalent levels of current. The cathodes are biased to  $+18V$  using separate common cathode resistors. The  $5K\Omega$  impedance plate-to-plate OPT presents each pair of tubes with a  $1.25K\Omega$  load impedance (with a matched secondary load) for signal currents in Class B region, and  $2.5K$  in Class A region.

The supply voltage  $VS1$  to the output valve plates is about  $245V$ . Plate-cathode voltage will be lower than  $VS1$  by an amount up to  $\sim 20V$ ; ie. OPT half resistance of about  $76\Omega$  with an idle current of  $0.03A$ , and  $18V$  cathode bias. As the output loading increases, the supply voltage  $VS1$  to the output valve plates sags to about  $220V$  [check]. Plate DC voltage will be lower than  $VS1$  by an amount up to  $\sim 34V$ ; ie. OPT half resistance of about  $76\Omega$  with a peak current of up to about  $0.12A$ , and  $25V$  cathode bias.

Screen voltage supply  $VS2$  will vary from about  $200V$  towards  $180V$  under steady-state heavy load. Screen voltage lower than  $VS2$  by  $18V$  at idle, and  $\sim 35V$  due to the  $330R$  stopper resistors at up to  $30mA$  screen current per tube, and the cathode bias voltage. Peak screen power dissipation is then up to  $30mA \times 150V = 4.5W_{pk}$ , and about  $180 \times 0.008 = 1.4W$  average.


The maximum output valve bias current allowed is dependant on the maximum recommended plate dissipation of  $7W$ ,  $+ 3.2W$  for the screen, for the 6BM8:  $I_{bias(max)} = P_d / V_b = 7W / (220-20V) = 35mA$ .

Assessing the 6BM8 plate curves, which shows the  $7W$  constant power contour, indicates how the amp will dynamically exceed plate max design dissipation levels. Note that these curves are for a

200V screen level, with no compression influences, and the load lines are for 2.5K (5K P-P transformer push-pull) moving to 1.25K.

For a peak plate current of 130mA, then the nominal output power of the amplifier would be:  $(I_{pk})^2 \times R_{pp} / 8 = 0.13 \times 0.13 \times 5k / 8 = 10.5W$ . For this maximum signal condition, the rms OPT current draw is likely about 83mA (64% of peak), and the average VS1 power consumed is about  $230 \times 0.083 \text{ Arms} = 19W$ , and the OPT loss is about  $(0.083)^2 \times 153\Omega = 1W$ , and cathode bias loss is  $(0.083)^2 \times 300\Omega = 2W$  so the tube plates dissipate  $19 - 2 - 1 - 6 = 10W$ , or just under 5W each, which is ok.

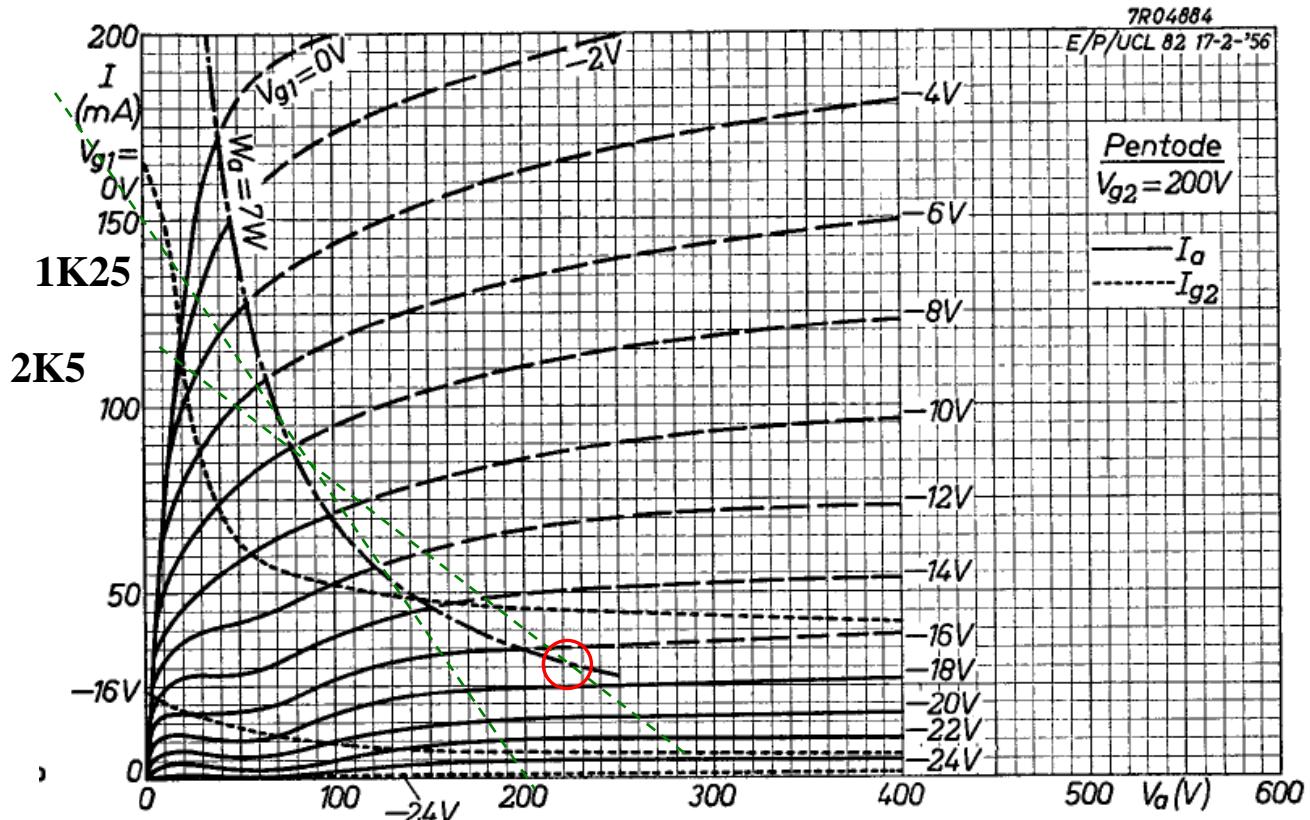Cathode bias trimmed to 30mA nominal with 600R resistance and nominal 18V bias. However, general comment is that common bias sounds better, but then valves would need to be better matched.





### 3.4 Power Supplies

The full bridge rectifier circuit uses a 200V secondary HT winding. Only one 6.3VAC secondary is available for heaters. Heater loading is  $0.3A + 2 \times 0.78A = 1.8A$ .


C11A is replaced with a 120uF 400V cap. The ripple voltage across V1 is mainly 100Hz, at a measured level of 1.24Vrms at idle.

Bleed: 100k on VS1.

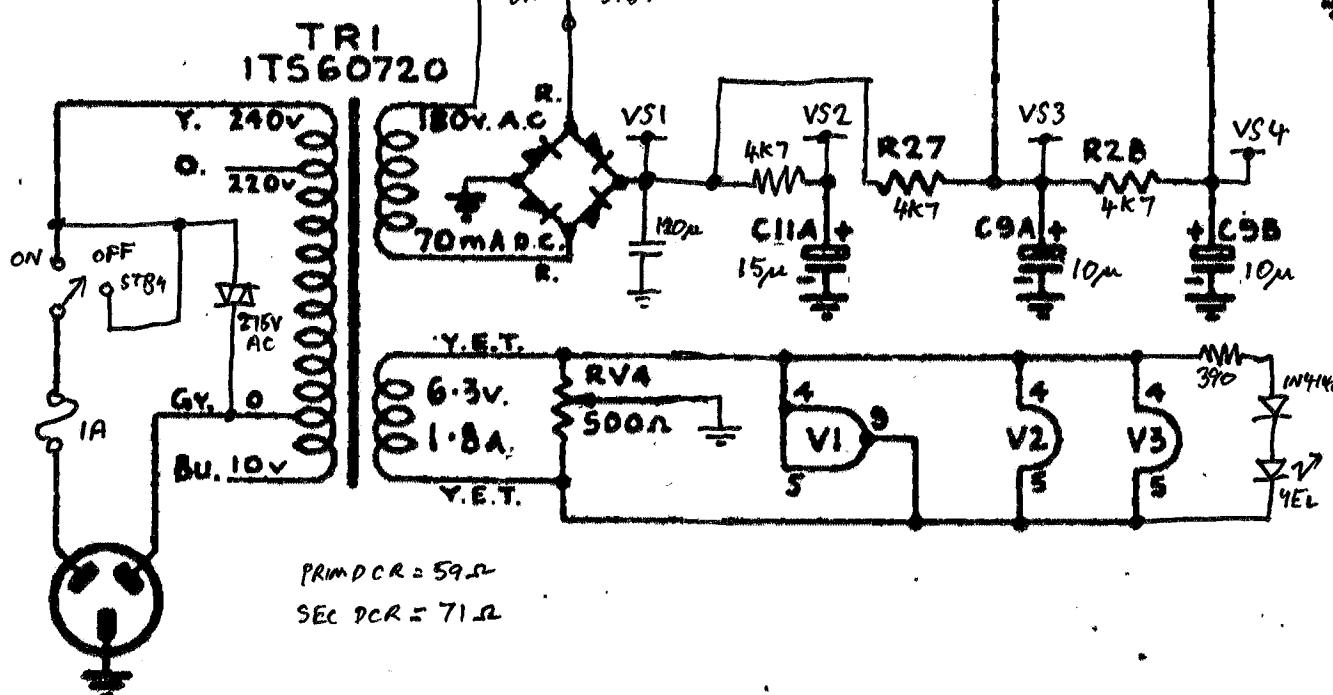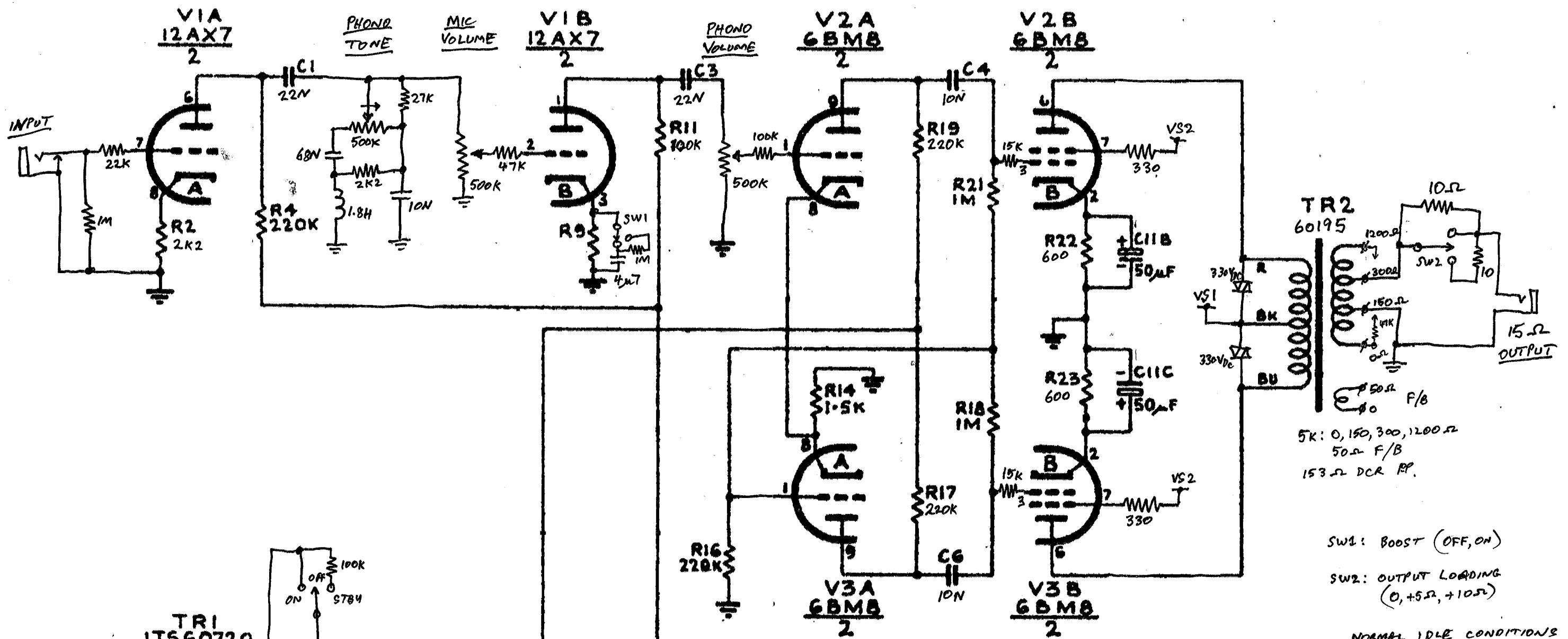Distributed star 0V with one link to chassis at power supply.



CHASSIS LAYOUT  
VIEWED FROM BACK.

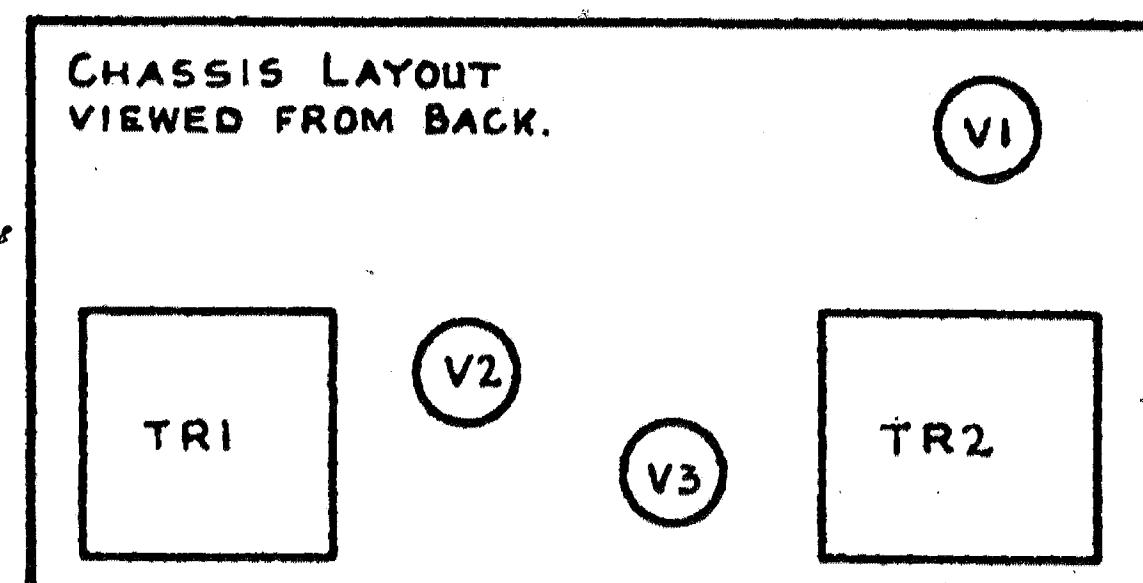

SERIAL N<sup>o</sup> A42976



8 WATT AMPLIFIER  
TYPE 1G59774  
DRG. 59774C1

PA 774