

Fig. 5—A graph showing the variation in harmonic distortion at various power output levels in the Bogen model DB20.

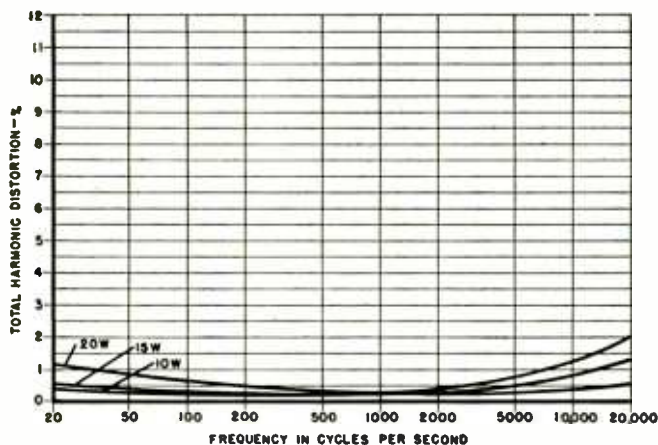


Fig. 6—Harmonic distortion in the DB20 at the 10-, 15-, and 20-watt levels for frequencies up to 20 kilocycles.

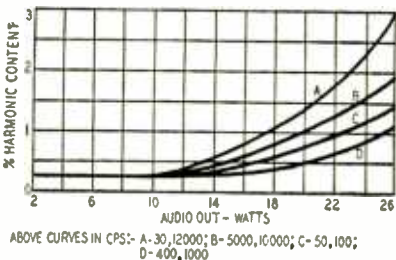
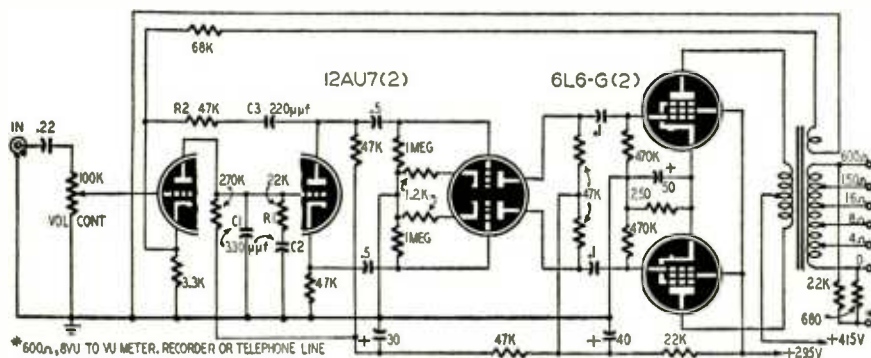


Fig. 7 (above)—The Stromberg-Carlson AR-425 amplifier in the schematic has a sensitivity of 2 volts input for full rated output. Fig. 8 (left)—A graph of the harmonic distortion variation in the AR-425 amplifier at different frequencies as well as power output levels.

specified level of distortion without critical balancing of the output stage.

### Stromberg-Carlson model AR-425

The power-amplifier section of Stromberg-Carlson model AR-425 custom amplifier is shown in Fig. 7. A direct-coupled phase inverter circuit is used, but the push-pull voltage-amplifier stage does not have a common cathode resistor and close-tolerance resistors are not used for balancing. A simple beam tetrode power stage is used in this amplifier, with no intrastage feedback, yet the harmonic distortion at 20 watts output is approximately the same as in the other amplifiers described in this article, according to curves furnished by the manufacturer (Fig. 8). Using frequencies of 60 cycles and 7 kilocycles in a 4 to 1 voltage ratio, this amplifier develops only 0.7% intermodulation distortion at 15 watts output. Using 40 cycles and 7 kc, the intermodulation distortion is 1.2% at 15 watts. When making power runs to determine the percentage of intermodulation distortion, the 15-watt complex waveform measured by the distortion meter is equivalent to 23.5 watts of sine-wave signal having the same peak value as the resulting signal produced by intermodulation within the audio amplifier.

The low distortion is accounted for partly by the large amount of over-all negative feedback used. To overcome the resulting tendency to oscillation at high frequencies, the gain of the first two stages at high frequencies is reduced by two separate means.

The output of the first stage is shunted by a combination of two capacitors and one resistor, C1, C2, and R1, so that the effective load impedance at high frequencies is reduced. Also, negative feedback at high frequencies is provided between the plate of the second stage and the cathode of the first, through C3 and R2.

All four of the amplifiers discussed in this article have damping factors of around 15, compared with 30 for classical triode versions of the Williamson. That is, the various tetrode versions have an output impedance of about one-fifteenth the speaker voice-coil impedance, against one-thirtieth for the triode circuit. Williamson points out<sup>1</sup> that the effective damping resistance is the sum of the amplifier output resistance and the speaker voice-coil resistance. The tetrode circuits therefore have total damping resistances, not twice as great as the triode circuit, but only about 3% greater. END

### References

- "Amplifiers and superlatives—an examination of American claims for improving linearity and efficiency," D. T. N. Williamson, and P. J. Walker. *Wireless World*, September, 1952, p. 357.
- "Design for a high-quality amplifier," D. T. N. Williamson. *Wireless World*, April, 1947, p. 118, and May, 1947, p. 161.
- "An ultralinear amplifier," D. Haffler and H. I. Keroes. *Audio Engineering*, November, 1951, p. 15.
- "Ultra-linear operation of the Williamson amplifier," D. Haffler and H. I. Keroes. *Audio Engineering*, June, 1952, p. 26.
- "Review of British Amplifiers," J. Moir, FM-TV, October, 1951, p. 30.