

This article discusses protection topics related to a valve amplifier's output transformer.

Over-current and over-voltage stresses are common causes of output transformer failure, so these two topics are discussed in detail. The influences that can cause stress are described, along with common techniques for managing those stresses. Fuse and PTC selection for over-current is discussed. MOV selection for output transformer over-voltage protection is presented as a simple addition.

Measurements are presented on two amplifiers showing results in an X-Y plot condition over a period of time, and in separate plate voltage and current waveforms during a short signal burst.

Techniques to test for a failed output transformer are described.

Protection of power transformers and chokes used in valve amplifier power supplies is also discussed.

Contents

Over-current Protection	2
Fault causes	2
Fault current level influences	2
Fault current protection techniques	3
PTC over-current protection	4
Over-voltage protection	5
Stress influences	6
Managing over-voltage stress	7
Using and selecting MOVs	10
Other forms of over-voltage stress	12
Measurements	13
Testing for a failed OT	16
Power transformer and choke protection	18
Over-voltage protection	18
Over-current due to failed valve diodes	18
Over-current due to failed parts	19

The output transformer (OT) is expensive to replace, and finding an authentic replacement may be a struggle, so adding extra protection is a wise move when restoring, improving or cloning an amplifier and may also help protect the power transformer (PT) as well.

Although output transformers are a pretty tough part, there are many stories of amplifiers with a failed or replacement OT, or no OT at all.

Like all parts, adequate cooling is required for the OT. Some amplifiers have a poor layout of transformers and valves, with parts sandwiched together in close proximity, and with limited ability for free air movement to allow removal of heat. Some old amplifiers that were intended for PA use, with output power only intermittently needed, were borderline examples. When restoring for modern day use as a guitar or bass amp, then be aware of the likelihood of the amp having a higher continuous output loading than originally intended, and be often cranked into over-drive.



Figure 1. Amp purchased with no OT.



OT sandwiched between output valves and barriers.

Electrical protection of an OT is commonly achieved using over-current and over-voltage protection techniques.

Over-current Protection

Over-current protection of the OT primary winding as in a single ended (SE) output stage, or primary windings as in push-pull (PP) or ultra-linear (UL) output stages, is often just by a power supply fuse on the mains input. Typically, there is a direct connection of the high voltage DC power supply to the OT, either to one end of the OT primary as in a SE stage, or to the primary centre-tap (CT) as in a PP stage. As such, a fault in the output stage may cause a damaging current level to flow.

Fault causes

One example of an over-current inducing fault cause is the loss of bias voltage in a fixed bias amp which would cause maximum continuous tube current conduction in both half-windings of a PP output stage (loss of bias can be simply from a poor pot wiper or broken pcb trace).

Another example is a leaky coupling capacitor between driver and output stage, which can force an output valve grid positive in voltage, and hence also cause a loss of bias to an output stage valve. Similarly, a failing grid-leak resistor on an output valve, or an output valve going 'gassy' (whether by a leak, or by excessive outgassing under red-plate operation) can lead to the grid voltage going more positive, and hence a loss of bias voltage, with the current in that valve increasing uncontrollably.


There is some evidence to show that output stage valve screens can short to cathode or other internal electrodes, as is likely when screen dissipation limits are exceeded, and the screen wire sags or breaks.

Failure of heater-to-cathode insulation in a cathode biased output tube can force that tube into full conduction if the heater is grounded (as the bias is forced to 0V). For this type of fault, both tubes in a PP stage with common cathode biasing would also fully conduct.

Another failure mode is when OT primary current shorts or arcs from an output stage anode pin 3 to the heater pin 2, and then through the heater circuit to ground (see next section for cause). In a somewhat similar manner, a valve with a broken base peg could be incorrectly inserted, which could connect an output stage anode circuit to cathode circuit through the valve heater.

Faults can even occur during servicing – note pin in photo.

A meter probe accidentally shorted pin 3 of an output valve to a nearby grounded socket holder's earthing tab when the amp was on. The OT half-primary winding inductance ensured the arc continued, even when the probe was quickly removed, and the arc continued for a few seconds eating away at the pin 3 terminal and cracking the ceramic edge, until the only fuse in the amp (PT mains side) blew. The OT survived in this particular case!

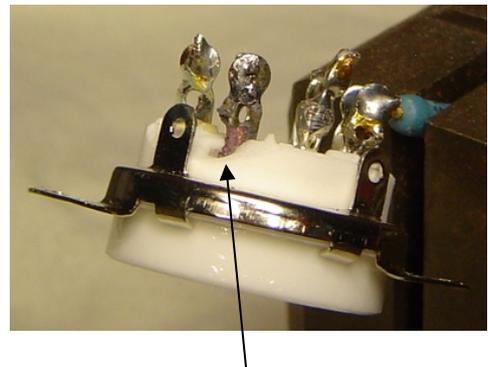

Fault current level influences

A 'prospective' fault current level can be estimated or even simulated with PSUD2 using known or measured resistance values of parts in the fault current path.

A fault on the B+ supply line is likely to reach the maximum prospective current that the power supply can deliver. PSUD2 is great for indicating that fault current level, as it takes in to account primary and secondary winding resistances in the PT, and in the rectifier diode, as well as the sagged B+ voltage, and can calculate rms current level through the fault resistance path.

Fault current that passes through a heater supply can be very influenced by the type of heater supply grounding configuration used. A heater winding with CT connected to ground (or one end of heater grounded) imposes a very low resistance path. If the heater is grounded through a fixed resistor humdinger, or humdinger pot, then the series resistance to the fault would be increased, but is likely to still

be low, as both sides of a humdinger connect to ground. An elevated heater could introduce a relatively high resistance fault path from a resistive divider elevated supply, or a relatively low resistance path if using for example a common cathode voltage of an output stage. A heater supply with high resistance to ground could cause the heater supply to be elevated towards HT B+ level if a fault occurs, and lead to heater-cathode failure of all valves in the amp.

Fault current protection techniques

Depending on the PT and OT, and fault, the fault current could damage the PT before damaging the OT.

If at all possible, a power supply fuse on the secondary side of the PT should be included as it offers better protection than just a single fuse on the primary side of the PT for the many types of fault that can occur in an amp. A procedure for selecting an appropriate fuse is provide in the link - [Valve amp fusing](#).

For larger amplifiers, especially those that run parallel valves in the output stage, the addition of a fuse in each valve cathode 'leg' provides better protection as each cathode fuse rating can be made significantly lower than the secondary side PT power supply fuse rating. Even a low wattage current sense resistor used for idle current bias adjustment for each cathode could be used as a 'poor man's fuse' – however the resistor needs to have a wattage rating just suited to the overdrive conditions¹. Some hi-fi amps even capacitor bypass the fuse, or sense resistor and fuse, to minimise their influence on signal performance.

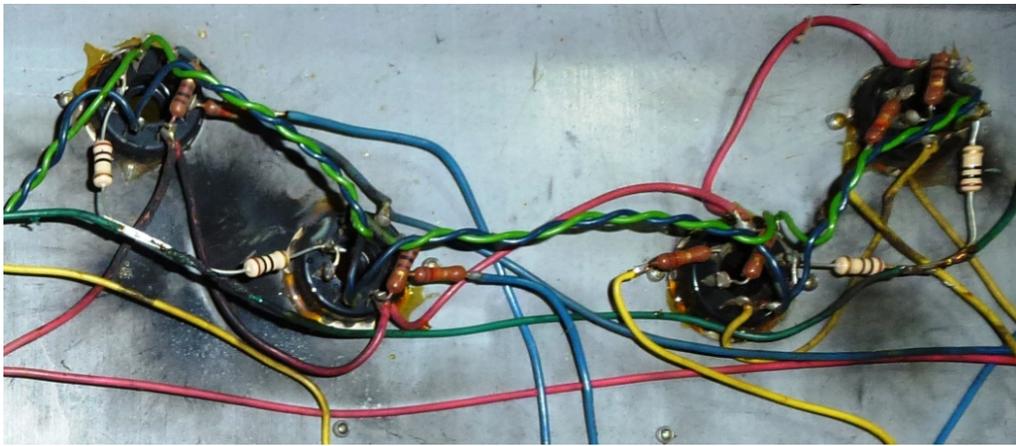


Figure 2. Poor man's fusing probably saved the OT in this repaired Phone amp.



Figure 3. 10Ω metal film for cathode current sensing. "Popped" by a bad 6GW8.

A parallel 150V Zener diode across each cathode 'fuse' is one option. If a cathode fuse fails, and the valve itself is still ok, then the Zener diode aims to keep the cathode from rising more than the valve's cathode-to-heater voltage limit (200V for most valves, although 100V for EL34, and 150V for the KT's). If a fault causes a high current to start flowing in the cathode circuit, V_{ak} will be low with the fuse still intact. When the fuse fails, V_{gk} will go negative as cathode voltage increases, and V_k will increase (to the Zener voltage). If the bias supply had failed then the grid may be up to 0V (and $V_{gk} \sim 0V$ would cause the high fault current).

¹ Overload testing on some 0.6W MF MRS25 1Ω and 10Ω resistors showed they could still 'function' even when subjected to 15x their dissipation rating (ie. 9W, or 3A for 1Ω, and 1A for 10Ω), with the acrid fumes being an indicator of a fault. Only some manufacturers make 1Ω MF resistors in 0.4W or 0.25W ratings, whereas 10Ω 0.25W is appropriate for cathode sensing to 160mA continuous (ie. class A, or 320mA with 50% duty-cycle).

If the grid is stuck at 0V, then Vgk falls to ~ -150V (ie. deep cutoff), so little current flows through the Zener diode, and a normal 1-5W Zener would dissipate little power. If the valve were damaged with a short to cathode, and the fuse opened, then the Zener would likewise be damaged (but it is <<\$1, so is a fair trade-off). Modern amps (eg. Orange, Marshall) use a LED and series resistor across their cathode fuse, both to act as an indicator of a blown fuse, and to constrain cathode voltage rise.

Fusing of the HT (high tension) DC voltage from the power supply to the OT is not recommended as high DC voltage is prone to tracking across fuse holders and normal 20mm and 3AG fuses don't have DC voltage ratings and may well shatter. If such a fuse blew, then it may also generate a high-voltage spike across the OT, depending on the circuit. In addition, if a pentode output stage still has screen voltage applied after the plate voltage has disconnected then the output valves will likely get damaged.

A fault such as a pin 3 to pin 2 arc, can force a fault current through an output stage valve's heater to ground. A humdinger (fixed resistors or trimpot) can act as a poor man's fuse to stop the fault current, but the heater-cathode voltage limit needs to be constrained. One option is to connect a 150V Zener with back-to-back 1N4004 diode from a heater side to ground.

Cathode biased output stages, and screen 'stopper' resistors can significantly suppress fault current levels for some types of over-current fault. Adding screen stoppers in an old amplifier that had none in place can be worthwhile to reduce OT over-current stress in UL stages, or triode connected pentode PP stages, as well as PT stress if the screen internally shorts. Typical parts used for protection in a fixed bias PP stage are shown in Figure 4 below.

TYPICAL ADDED CIRCUITRY

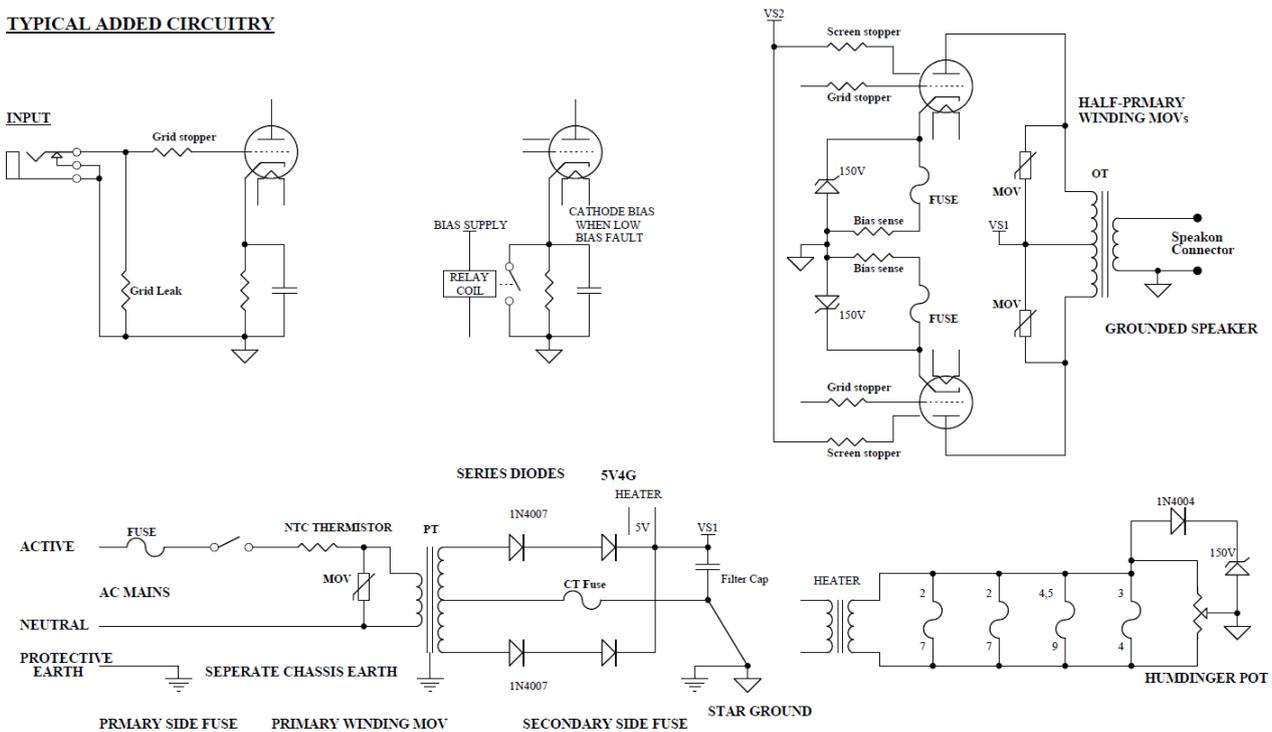


Figure 4. Typically added circuitry for protection.

Of note is GEC's technique for bias loss, where a relay contact shorts out a protective cathode bias resistor during normal operation. If bias is lost then the relay contact opens, and the output stage operates with cathode bias. An alternative to an electromechanical relay is a modern optomos form B device - an LCB110 has < 10Ω contact resistance (DC only configuration) and only needs about 2mA of LED current.

PTC over-current protection

A positive temperature coefficient (PTC) varistor may be a suitable over-current protection technique. The PTC can provide a negligible 'cold' resistance, that then rapidly increases to many kΩ (the 'trip' region) as the PTC reacts to an over-current, and so will raise the cathode voltage V_k and suppress the over-current.

Somewhat like a fuse, the time taken for the part to heat up to the trip point (typically 70-80°C) where the resistance starts to rapidly increase, depends on the ratio of over-current and the physical mass of the part. Depending on the fault current characteristic with V_k , the part will reach a thermal equilibrium in the 'trip' region with a constrained fault current level assuming the fault persists. Although some PTCs have voltage ratings above 100V, the readily available and cheap PTC's used in solid-state power amplifiers typically come with a voltage rating up to about 60-85V, in which case it would be appropriate to parallel the PTC with a Zener diode to both maintain the integrity of the PTC and to restrain the cathode voltage rise. A main concern with using a PTC is to isolate it from experiencing a high ambient temperature, as the current level at which the PTC trips is very dependent on ambient temperature, and the PTC may trip at a significantly lower current level than expected, and hence impose on normal amp operation.

PTC parts like [Littelfuse's RXEF series](#), have 'HOLD' current ratings from 50mA to many Amp, although up to a 0.5A HOLD rating should cover most valve amp applications. For example, a KT88's cathode current may peak to 0.5A for 50% duty cycle as an extreme operating condition, such that the average power dissipation in a PTC is equivalent to a constant 0.25A. An RXE050 with a 0.5A HOLD rating (ie. 50% HOLD margin) has a nominal cold resistance below 1Ω, and would trip for a continuous fault current above 1A (in 40 secs at 20°C). But note that the Hold and Trip current ratings are in a 20°C ambient, and would be nominally derated to 80% if local ambient reached 40°C, and to 60% at 60°C, and so the HOLD margin may be significantly reduced. Also note that the trip time is nominally 2 secs (4 sec max) for a 2.5A fault level from 20°C, and nominally 1 sec for 3.5A (7x the Hold current).

As a general characteristic, a PTC part's resistance remains fairly constant from around 20°C to about 80-100°C (depends on the part model), as the part temperature rises with any current increase in the HOLD region. A parallel capacitor can be added if needed to minimise any unwanted signal voltage developed across the PTC.

If a Zener diode was added in parallel to the PTC to restrict the fault level voltage at the cathode, then the prospective fault current level with the cathode at circa 60-80V needs to be assessed, as the Zener could then fail open-circuit and the PTC could then fail. PSUD2 can be used to estimate the cathode voltage during a fault by modelling the PTC as a high resistance.

As an example of PSUD2 assessment, the [article on fusing an amp](#) includes assessment of a [VASE 100W amp](#) with a KT88 fixed bias PP output stage when output bias is lost and both KT88's conduct. Each anode fault path presents about 600Ω as the anode operating point is past the datasheet I-V knee in the constant current region. The total loading on the power supply is then about $(600+36)/2 = 318\Omega$, and the cathode current could initially rise to at least 0.5A as the power supply is quite stiff. The secondary side winding current would be about 4Arms, and a 1A T IEC secondary side fuse would blow in the range 150ms to 3 sec. An RXE050 PTC in each KT88 cathode would likely take tens of seconds to trip (eg. if no secondary side fuse), and its voltage could then rise in excess of the PTC voltage rating although that would then force V_{gk} to a large negative voltage and restrain cathode current to below 10mA, and so a 68V 5W Zener should be adequate protection. In this case the PT secondary side fuse provides better discrimination to protect each half-primary winding of the output transformer which has to survive about $36\Omega \times 0.5A = 18W$ dissipation.

Another fault scenario for the VASE 100W amp could be a short from plate or screen to cathode. The fault current may then be quite high (>3.5A) and so a PTC may trip within 1 sec. In this case the PT secondary side fuse should blow within 20-40ms, so provides better discrimination.

Over-voltage protection

Over-voltage protection of an output transformer (OT) is a much more complex topic. OT's typically have windings in layers separated by insulation, with each turn of wire insulated from the next turn by the winding wire's enamel coating. Layer end turns and lead in/out wires have defined creepage and clearance distances to other conducting parts. Insulation between layers and creepage/clearance performance can break down if voltage levels become too high. A breakdown of insulation can subsequently cause arcing between turns, or between layers, or between layers and core, or between lead-in wires and winding layers, leading to local heating and either a local short-circuit or an open-circuit within a winding.

dalmura.com.au/projects/

Stress influences

OT primary winding over-voltage conditions can arise from:

- instability oscillations.
- abrupt changes in primary or secondary winding current causing the inductive winding energy to transfer to the winding's self-capacitance and connected capacitances, and to other windings, and raise the voltage across the winding(s).
- being forced by speaker emf applied to the secondary winding.


Instability oscillations are mainly due to poorly managed or inadvertent feedback of the amplified signal (either at the OT primary or secondary windings) to an earlier stage. Many guitar amps don't use feedback around the output stage, but poor wiring layout or poor placement of the OT can sometimes cause induced feedback into sensitive high-impedance points of preamplifier stages. Gross instability could stress the OT and is likely to be noticed as distortion or noise of some kind. As an example, AWV investigated field reports of KT66 base flashover failures circa 1950, only to find that constructors had overlaid grid and anode wiring to make a "squegger" oscillator.

Abrupt changes in OT primary winding current can occur for a myriad of reasons, for example:

- when a conducting output valve fails open circuit.
- when an output valve(s) is forced to a short-circuit condition which then blows a fuse.
- when an arc-over occurs on a valve base (eg. between anode and heater pins 2 and 3 in many common output stage valves), or internal to a gassy valve.
- when a speaker lead is accidentally disconnected or a poor quality plug/socket gets twitched or a speaker impedance selector is used or a selector switch contact arcs.
- when a 'speaker protector' such as a fuse blows.
- when a speaker fails and goes open-circuit when over-driven.
- when a speaker is left unconnected, and the output stage is over-driven, then plate current can reach high levels prior to being driven off fast.
- when cross-over distortion causes one valve in a push-pull stage to be driven into cut-off, when the other valve is already in cut-off.

If an abrupt change of current in a transformer winding occurs, then the energy in that winding looks for other ways to continue to flow. In a transformer, energy transfers from one winding to another winding when the other winding continues to allow power to flow at the same rate (ie. the other winding is loaded), and there is good coupling between the windings (ie. leakage inductance of each winding is low, as is typically the case for OPTs). If no other windings are loaded, then the inductive energy in a winding transfers to raising the voltage across the winding's self-capacitance ($CV^2/2$) and any connected parasitic capacitance, as well as coupling to the shunt capacitance of other windings. Even when other windings are loaded, energy in the leakage inductance of the winding may cause a transient voltage.

Most of the reasons above are related to a one-off fault situation, when just a single overvoltage event occurs. In contrast, situations that relate to cross-over distortion or no-loading may cause repetitive over-voltage transients. Cross-over distortion drives the PP stage valves into cut-off at the same time, such that the OT primary windings are not loaded for a short period of time. In that situation, the speaker coil's emf voltage may be capable of forcing primary voltage transients. Unloaded windings due to a disconnected speaker, along with high drive signal levels at the output stage, may force primary voltage transients to exceed $2xB+$, for example in a PP output stage this could also push an anode to below 0V on the other half-winding.

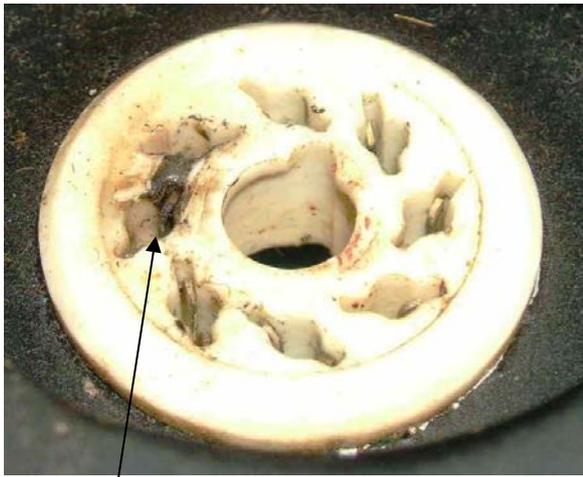

Arc-over from heater to anode [thanks Ian]



Speaker fusing is not common – with good reason!

Figure 5. Some practical examples.

For the example of an abruptly disconnected speaker lead, the inductive energy in the OT secondary winding could couple to a primary winding that has a valve conducting, and hence the energy has an escape path that would not likely cause a problem. In a PP output stage, if the primary winding valves were in cut-off (eg. due to crossover distortion) at the time of the fault then the inductive energy in the faulted winding has no other option than to couple to all OT windings and raise all available stray capacitances within the OT to a high voltage spike level. The inductive energy ($0.5 \times L \times I^2$) is transformed to a voltage rise V across stray capacitances in the OT windings ($0.5 \times C \times V^2$).

A similar example would be when a conducting valve fails abruptly. The current in the primary winding associated with the failed valve forces inductive energy to want to transfer elsewhere. If a speaker is connected then the secondary winding may provide a low-impedance path for the energy to couple to, although the speaker impedance is likely to be high for a single fast transient.

Managing over-voltage stress

Some circuit designs provide a noticeable loading on OT windings, especially in the context of suppressing high voltage spikes. A resistor-capacitor RC conjunctive filter circuit, or a capacitor, are sometimes applied across an OT primary winding (for PP stages this can be from plate-to-plate, or plate to CT, or plate to ground). These filters were often used to retain stability in amplifiers with feedback, or to shape high-frequency response, but can also provide a significant 'snubbing' effect on any voltage spike level generated across a winding.

Over-voltage protection was sometimes included in amplifiers, especially Public Address (PA) amplifiers. Two examples of the 'spark gap' technique, shown in Figure 6, show the gap placed from plate to plate in a PP stage - although crude in form and not very accurate under varying humidity and dust conditions, it probably worked ok and was certainly appropriate for very high powered amplifiers [An approach to audio frequency amplifier design, GEC, 1957]. It may well have saved the OT shown in this thread ([video link now dead in thread](#)) when a newb foolishly checked if an old amp was still working.

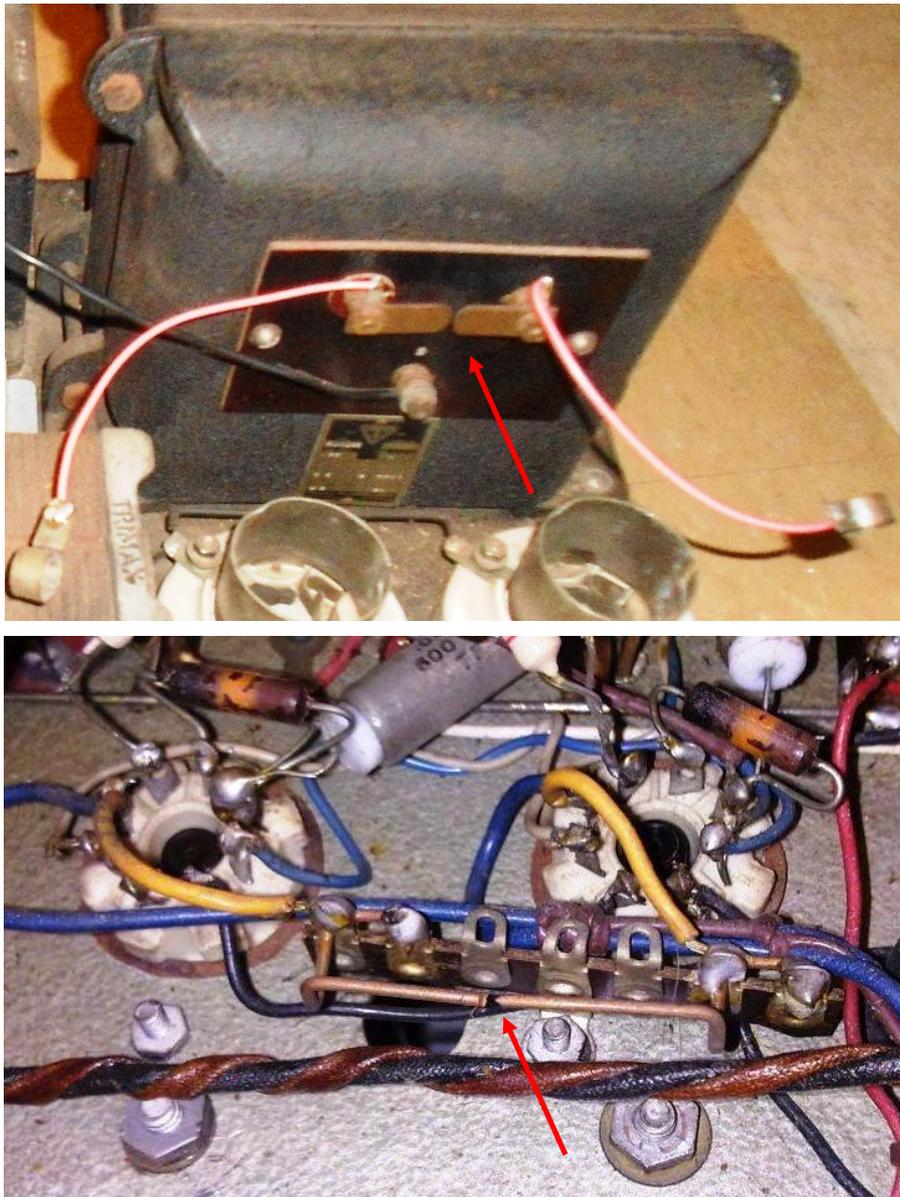


Figure 6. Examples of spark gap placed from plate-to-plate.

Gas discharge tubes were widely used in telecommunications for over-voltage suppression and have been seen in German Dynacord amps connected from plate-to-plate. The gas discharge tube has an arc voltage that varies widely with dV/dt and waveform, and once triggered will significantly clamp the voltage. Thyrectors (a type of semiconductor diode over-voltage protection device) were used in Traynor amps. Even gas regulator tubes like the OD3 were placed anti-parallel from plate to plate on a PP output stage.

A more common technique was a 'catch diode' placed from plate to ground, also known as a suppressor, flyback or free-wheeling diode. For older amps this meant using valve diodes, such as the two 6AL3 TV damper diodes shown in Figure 7 under the chassis in a circa 1960 Australian Sound and Television 100W A-series PA amp. Modern ss diodes are more robust, and this technique is by far the most commonly used in guitar amplifiers, for example Ampeg used two 1.4kV diodes in series from 1971, from 1980 Fender's use an R3000 diode (3kV 0.25A), Peavey use a SR2873, and Bugera use an R2000.

A disadvantage of the catch diode technique in a PP amp is that only one half-primary winding section is directly protected, with the other half-winding left locally unprotected. The half-winding with a voltage spike going below 0V relative to OT CT (sitting at B+ voltage level) causes a spike current to loop through the protection diode and the power supply main filter capacitor back to the OT CT as the main energy dissipation means.

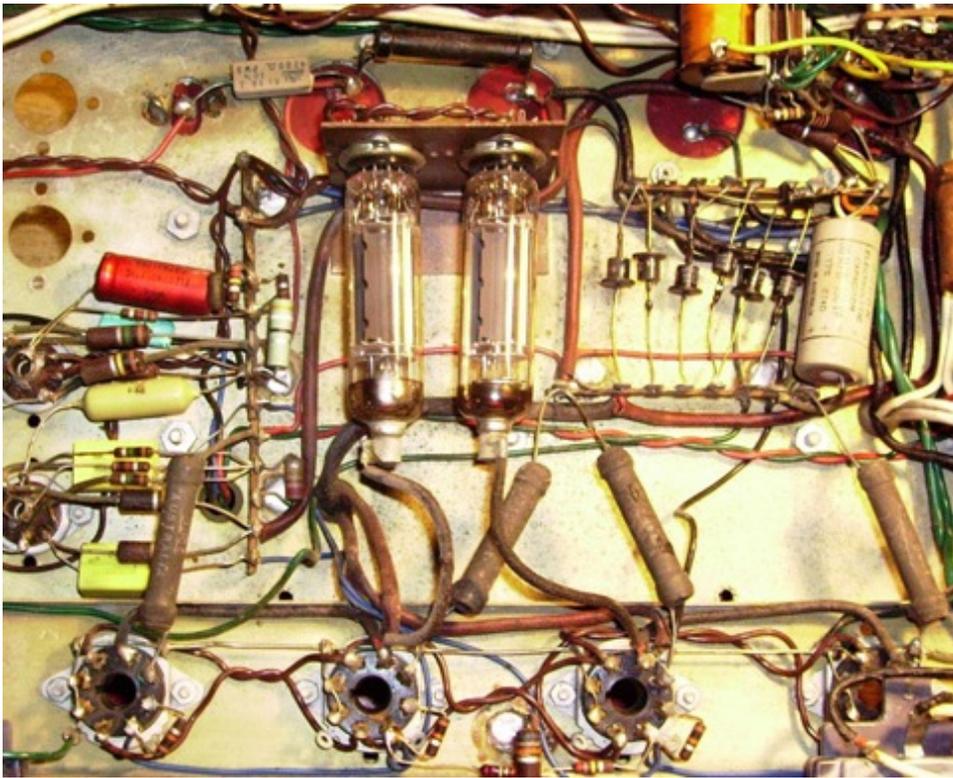


Figure 7. 6AL3 damper valves used as 'catch diodes' in a PP amp – and located underneath the chassis!

Another common technique is to place a loading resistor on the OT secondary winding. The added resistance needs to be high enough to not need a large power rating, and not divert too much power away from the speaker. This simple technique provides some suppression of any high voltage spike. Power loss is inversely proportional to resistance, so an 820Ω resistor loading a nominal 8Ω speaker impedance would dissipate about 1% of the amp's power rating (ie. a 2W resistor should be fine for most amps). If the speaker was disconnected, and a voltage spike across the loading resistor reached say 3x the peak level normally seen, then the loading resistor would transiently dissipate 10% of the amp's power rating. Apart from wasting part of the signal power, and slightly modifying the load impedance seen at the OT secondary, this technique is somewhat soft in nature in that it doesn't force a voltage limit, and choosing a resistance for the loading resistor is a subjective compromise, not an empirical science.

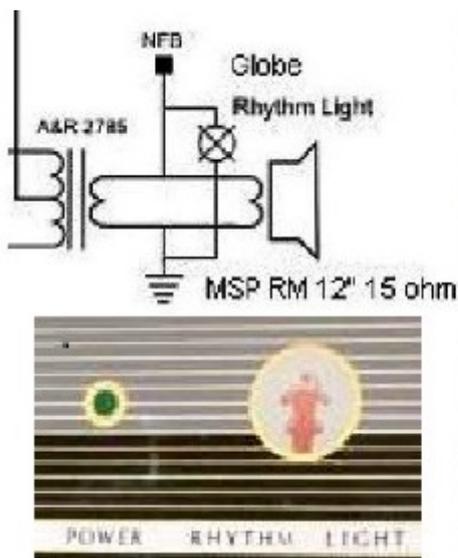


Figure 8. Goldentone made their OT secondary loading resistor into the RYTHYM LIGHT 'feature' on the front panel, which provides about 10% loading, and a touch of non-linear compression due to resistance change.

Another form of over-voltage snubber proposed back in the 1970's for a Vox AC-30 amplifier was a diode-resistor-capacitor circuit connected across the primary, with a series connection of neon bulbs across the capacitor to limit its voltage rise ([Everyday Electronics](#), June and July 1978 and Jan 1979).

An uncommon control technique to constrain anode voltage excursions was a signal level limiter type circuit seen in a few PA amps (AWA PA-30BZ, Philips EV4437A). A plate voltage excursion beyond a set level triggered a neon light that was coupled to a light dependant resistor that was used to attenuate the signal level prior to the output stage.

Using and selecting MOVs

In recent times, the metal oxide varistor (MOV) has provided another convenient technique for over-voltage clamping across an OT winding. The MOV is bi-directional and doesn't conduct current (ie. start loading) until exposed to a peak voltage above a nominal threshold (positive or negative going), and is cheap and available in a wide variety of voltage and energy ratings, so can be easily connected to an amplifier with negligible influence until the peak of voltage transients reach a high level.

The MOV only starts to clamp above a nominal peak voltage in a soft manner, and progressively presents a heavier loading to the peak if the transient energy is sufficiently large to keep pushing the peak voltage higher – which really suits the application. The MOV clamping voltage-current curve and tolerance is wide, especially if comparing it to a zener diode or some other kind of solid-state voltage clamp, although this is no disadvantage to transformer protection as there is normally a large voltage separation between typical winding peak working voltage levels and the typical voltage insulation rating provided in the transformer.

MOVs are typically used for AC mains protection, but most MOV data sheets provide DC voltage specifications (eg. the Littelfuse LA series at [Littelfuse MOV LA-34212.pdf](#)). An example 250VAC rated 7mm diameter disk MOV (eg. V250LA4 model) has a continuous DC voltage rating of 330V DC, and a DC voltage operating range from 354V to 473V at a current level of 1mA. Other relevant specifications for that example device are the capacitance of 90pF, the 21 joule rating for a single transient, some characteristic curves of how the clamping voltage increases with current level, and the indefinite repetitive surge current capability. What is missing is the average power dissipation below which no degradation occurs, which is about 0.25W for that size disk (0.4W for 10mmD; 0.6W for 14mmD, 1W for 20mmD from Harris).

The wide voltage range for 1mA DC conduction indicates the wide tolerance in peak AC voltage when a MOV starts to conduct current and hence starts loading a transformer winding. Eg. if a V250LA4 MOV was connected across each OT primary half-winding (plate to B+) as shown in Figure 4, plate voltage peak would need to swing at least 354VDC away from B+ for the MOV to start conducting 1mA (ie. the MOV would look like a 354kΩ resistor just at the peak of the waveform, but otherwise would effectively present an open-circuit to the winding). The same situation exists in a SE output stage for its single primary winding. Plate voltage can't typically swing closer than 50V to ground due to valve saturation, but could swing to 0V for unloaded conditions, so that particular MOV would normally look like an open-circuit for a B+ level up to about 350VDC with the output stage plate voltage swinging to squarewave unloaded clipping levels.

Some comments on MOV datasheets are worth making, as they can influence selection:

- the characteristic curves and max clamping voltage ratings are often for an applied AC voltage, so need to be interpreted with some caution, but do indicate the likely percentage increase in DC clamping voltage as MOV current increases above 1mA.
- The capacitance of a MOV device gets larger as disk diameter increases, and reduces as voltage rating increases (for the same disk diameter).
- The 'indefinite repetitive surge current capability' indicates the current level for a particular pulse width that can be passed without device degradation. The repetition frequency of such a pulse needs to be such that the average power dissipation within the MOV is within rating (7mm disk typically has a 0.25W rating).

The DC voltage rating at 1mA of a MOV placed across an OT primary winding should be above the maximum B+ power supply level (at high mains voltage and lowest idle current) by at least a good margin,

as the MOV should not be loading the OT for the normal situation where the plate pulls its voltage down from B+ to near 0V, or gets raised to twice the B+ level by transformer action.

Depending on what MOV voltage ratings are available, MOV's can be connected in series to double or triple the DC voltage rating so that it is high enough for the position. Eg. a 400VDC 1mA part becomes an 800VDC 1mA part when two MOV parts are connected in series. Only MOV parts of the same type/rating should be connected in series to make a higher voltage rated 'MOV'.

With respect to protecting the OT from insulation stress, a modern output transformer should be able to withstand at least 2kVDC from primary winding to core, and primary winding to secondary winding. Some manufacturers specify the test voltage they apply to confirm adequate insulation, but many don't. Although the transient withstand voltage across a winding is not typically specified, it is likely to be similar to the primary to core continuous rating. Choosing a MOV, or MOVs, with a 1.5 to 2kV DC clamping voltage for about 1A seems a reasonable selection target as that should provide a MOV DC 1mA rating that is well above the B+ level, and should constrain peak voltage across insulation to within a transformer's ratings.

For an amp with 500VDC B+, then two or three of the V250LA4 MOVs in series, connected across the OT primary winding would be appropriate (or across each half-primary in a PP stage). Two MOVs in series would start to load any transient voltage peak rising above 708V to 946V, and if the energy level in the transient was sufficient to force the winding voltage to about 1200Vpk then the MOVs shunt load the winding with $600 + 600 = 1k2\Omega$, passing about 1A at that peak. Three MOVs in series are also likely to clamp half-winding voltage to below 2kV, so may be the preferred arrangement. If a fault transient was a single pulse of width less than about 8ms, and current up to 1A, then the MOV experiences no degradation. If a repetitive transient was experienced, then MOV max average power level would determine if MOV degradation could occur.

If a MOV was placed across an OT secondary winding, the MOV AC voltage rating needs to be compared with the maximum AC signal voltage generated by the amplifier for the speaker impedance used, as the MOV should not be conducting when max output power is being delivered to the speaker. A 50W amplifier output into a 16 Ω resistor would generate an AC voltage of 28Vrms, indicating a MOV with at least 30-35Vrms 'continuous maximum Vrms' rating should be used. A speaker's impedance varies with frequency and so a 50Vrms MOV would be a safer rating (the LA range only goes down to 130Vrms, but Varsi have a range down to 11Vrms – www.varsisi.com).

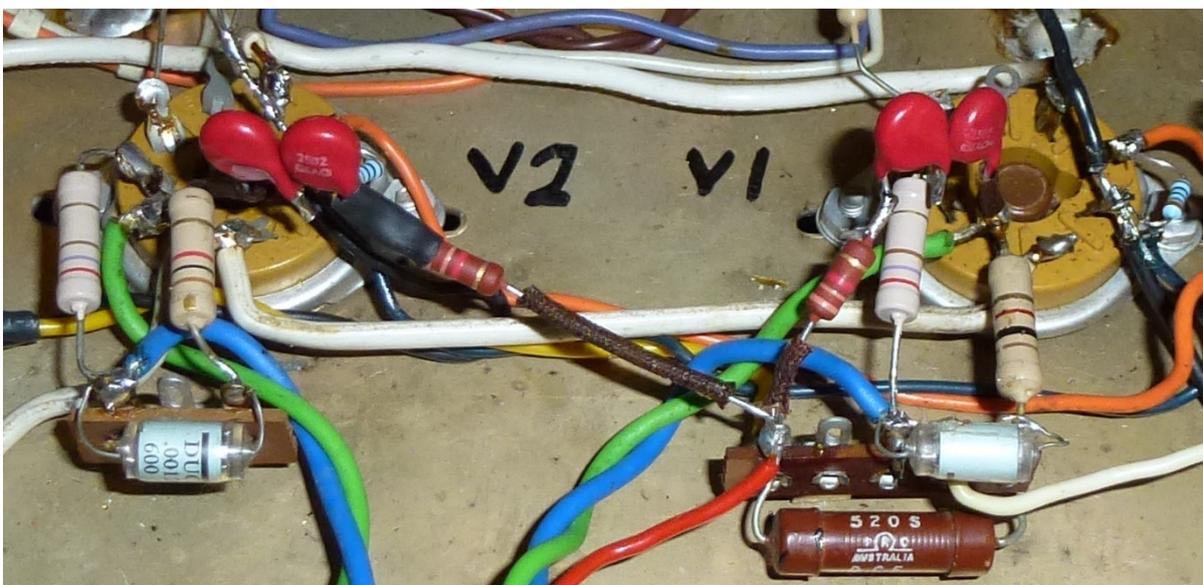


Figure 9. Ultra-linear PP stage (RTV&H 1960 100W PA amp). Original RC network from plate to screen. 1 Ω cathode sense resistors added. Series MOV-R circuit added to each primary half. No screen stoppers added.

As an example of the energy level in joules that may need to be clamped during a one-time fault event, the primary inductance of hi-fi OTs can exceed 100H (P-P). The inductance value is normally based on an

applied excitation sinewave voltage of about 5-10Vrms, so P-P inductance is likely to be substantially greater if a fault occurred when a high signal level excitation was present. However, if the fault scenario caused an over-current condition in the winding prior to the fault, then the winding inductance may have reduced dramatically due to core saturation.

An amplifier's operating current in an OT primary half-winding may peak at many hundreds of mA, especially for larger power amps. A fault event such as an open-circuit between valve anode pin and socket terminal could cause such a current level step. If a MOV bypass was used for protection, then the operating current level at the time of the fault would continue to flow initially into the shunt capacitances of the windings, and any loading on a winding, and if the winding voltage rose sufficiently then part of the decaying winding current would flow through the protection MOVs.

For a PP stage with 100H P-P inductance, and a half-primary winding current of 0.4A at the time of a fault, the energy in an OT half-primary winding is $(100H/4) \times 0.4A \times 0.4A / 2 = 2$ Joule. A single V250LA4 7mm diameter MOV has a 21 Joule rating, so any practical deployment of MOV's should cope well with that event, and may even experience no degradation depending on how the transient energy is apportioned to voltage rise on winding capacitances and loading on windings (such as a speaker).

The smallest disk size MOV I use is a 5mm S05K385 from Siemens (now TDK B722 series) with a minimum 620Vdc 1mA rating, and 40pF and 13J ratings. Care should be taken with such small parts to maintain a clean part surface between leads as the creepage distance is about 6mm and that may need to support transient voltages over 1kV, and could lead to arc tracking if the part surface was polluted.


A large fault winding current could flow if the anode shorted to a heater winding with a grounded heater CT, in which case current would be initially limited by OT half-winding resistance and $L \cdot di/dt$ rise time, and long term by effective PT source resistance and rectifier resistance, and any fault current fusing. High current may exist for some time until a power supply fuse blows. Winding current could be in the 1-10A range. The winding inductance could initially be high, but would fall with core saturation, so it is difficult to clarify if the winding energy would be substantially greater than for the previous 2 Joule scenario.

If more than one over-voltage protection technique is used, or MOVs are used on more than one winding, or MOVs are connected in series, then the energy being clamped would spread itself out to multiple protection parts, and hence each part would experience a lower level of power and energy dissipation than if only one part was trying to constrain all of a transient's energy.

The MOV capacitance could be a significant high frequency part for some hi-fi amp designs. Where this is of concern, a small diameter MOV model with multiple MOV's connected in series would minimise capacitance loading. In addition, a resistor can be placed in series with the MOV to form a conjunctive R-C filter. The series resistor could be at most a value similar to the winding impedance (eg. 25% of an OT primary impedance when used with a MOV placed from plate to CT), but is preferably a lower value so as not to cause a large increase in clamping voltage at the likely peak fault current that could flow. For example, a 5k Ω P-P OT could use a 1.2k Ω series resistor in series with a MOV across each half-winding, but this resistance value would drop 600V if transient MOV current reached 0.5A, in which case the example V250LA4 MOV clamping voltage would be 700-1,000V, so a lower series resistance of at most 470 Ω would seem more appropriate. Note that for this example MOV and a 1.2k Ω series resistor, the conjunctive filter corner frequency is over one megahertz.

Other forms of over-voltage stress

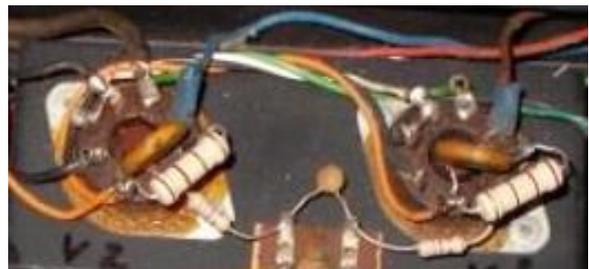
The OT windings connect to other parts that can also be stressed – in particular the output stage valve sockets have been known to arc between pins 2 and 3 (anode to heater) for typical power valves. Keeping the valve base surface clean between pins 2 and 3 is recommended, and some manufacturers glued spaghetti over those terminals and the OT wires.



Measurements


In the real world, the plate voltages in a PP stage do not lay themselves simply on a resistive loadline, but fly off to levels below 0V, and levels significantly in excess of twice B+, due to OT winding inductance, speaker load reactance and emf, and unloaded plate conditions when both valves are in cut-off.

Oscilloscope measurements shown below on a Fender 5F6A re-issue using 6L6 tubes (thanks to Loudthud on [Music Electronics forum](#) for permission to use his measurements and further discussions on them) clearly indicate the voltage levels experienced at the anode in a fixed-bias PP circuit. The first oscilloscope plot shows a trace for 6L6 plate voltage and cathode current for a sedate guitar input signal (display of the voltage trace is helped by the persistence of the oscilloscope screen). The plot shows superimposed 6L6 datasheet anode current versus grid voltage curves, along with a 30W plate dissipation curve.

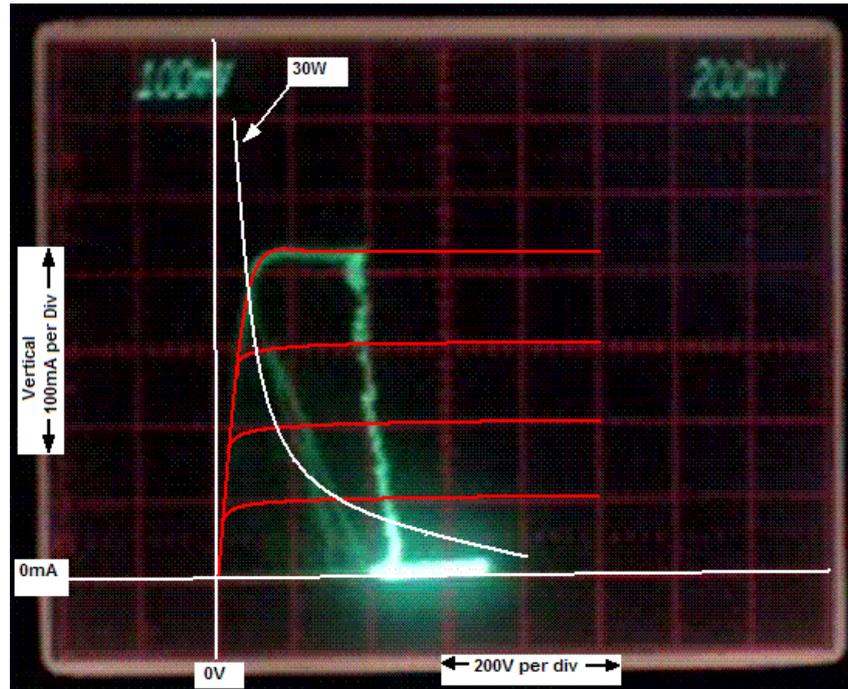


For a reference, the next plot below shows the 6L6 idle operating point at about 420V and 30mA. The 5F6A amp has a choke-fed screen voltage close to the idle anode voltage. The third plot shows the load line being followed when a sinewave signal is applied to a resistive load – the operating point moves away from the idle point, to a lowest anode voltage of about 80V and highest cathode current of about 400mA when being driven in to conduction by the signal, and to a highest anode voltage of about 720V at near zero cathode current when being driven in to cut-off. In this plot the anode voltage moves symmetrically below and above the B+ level (which would sag from 420V to about 400V) and indicates no sign of voltage stress on the OT winding. The peak anode current (and hence OT primary current) would be somewhat less than the measured 400mA cathode current, as the screen current contribution is seen to increase the trace's gradient noticeably as grid conduction conditions are approached.

Returning to the above scope plot, a faint resistive loadline ($320\text{V}/350\text{mA}=0.9\text{k}\Omega$, or $1.8\text{k}\Omega$ PP) can be seen extending from the idle point to the red overlay at about 350mA and 80V. That locus then follows the red plate saturation curve to a higher current ($\sim 420\text{mA}$) at a higher voltage ($\sim 400\text{V}$), when the locus falls to the idle point along effectively a low resistance loadline. This loadline profile appears to represent a low frequency signal with sufficient drive for the plate voltage to saturate, and also sufficient duration for OT primary winding inductance to fall (core saturation) with plate current maintained by the plate I-V curve at constant $V_g=0\text{V}$, as winding voltage falls up until when the drive signal turns off that plate current.

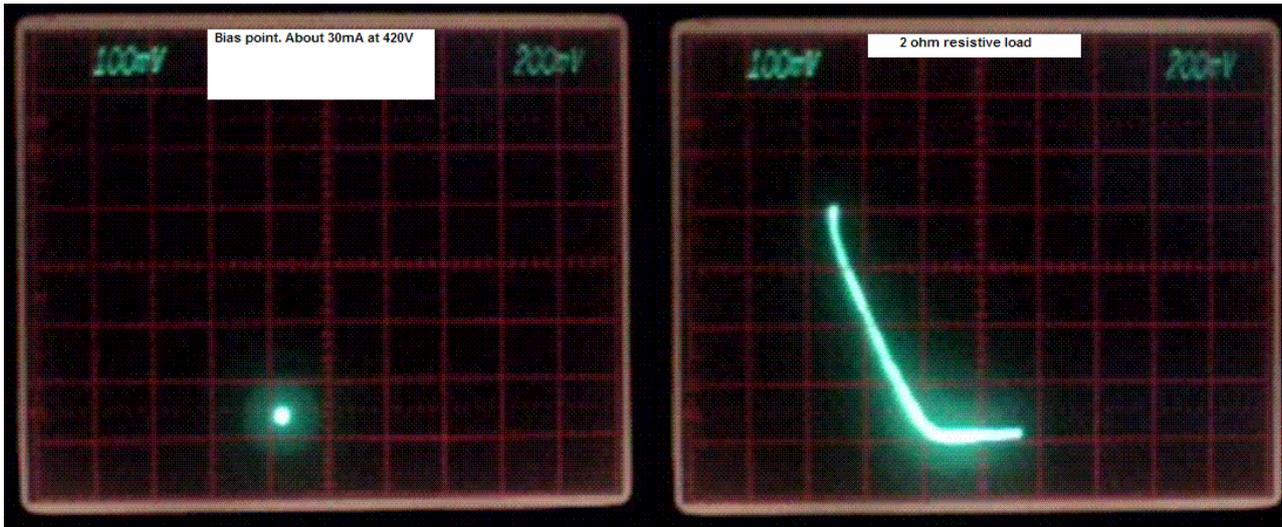

The 6L6 experiences more dramatic voltage excursions as shown below when a speaker load is used with a more aggressive guitar playing style, but still a long way from extreme over-drive conditions. The plot shows plate voltage extending down to at least -800V, and up to +1100V, which is about -1200V and +700V relative to B+ on the CT of the output transformer.

The 5F6A is likely to be experiencing blocking distortion under high signal level, which causes crossover distortion that would force both valves into cut-off at the same time for a portion of time. The plot below indicates a square-wave type plate operation, with an unloaded horizontal plate voltage falling from idle, followed by plate current rising along the $V_{g1}=0V$ vertical curve to a high plate current period, followed by V_{g1} falling and plate current and voltage falling back to idle or cut-off conditions via many different paths (likely due to remnant energy in primary winding leakage inductance or speaker cone movement).

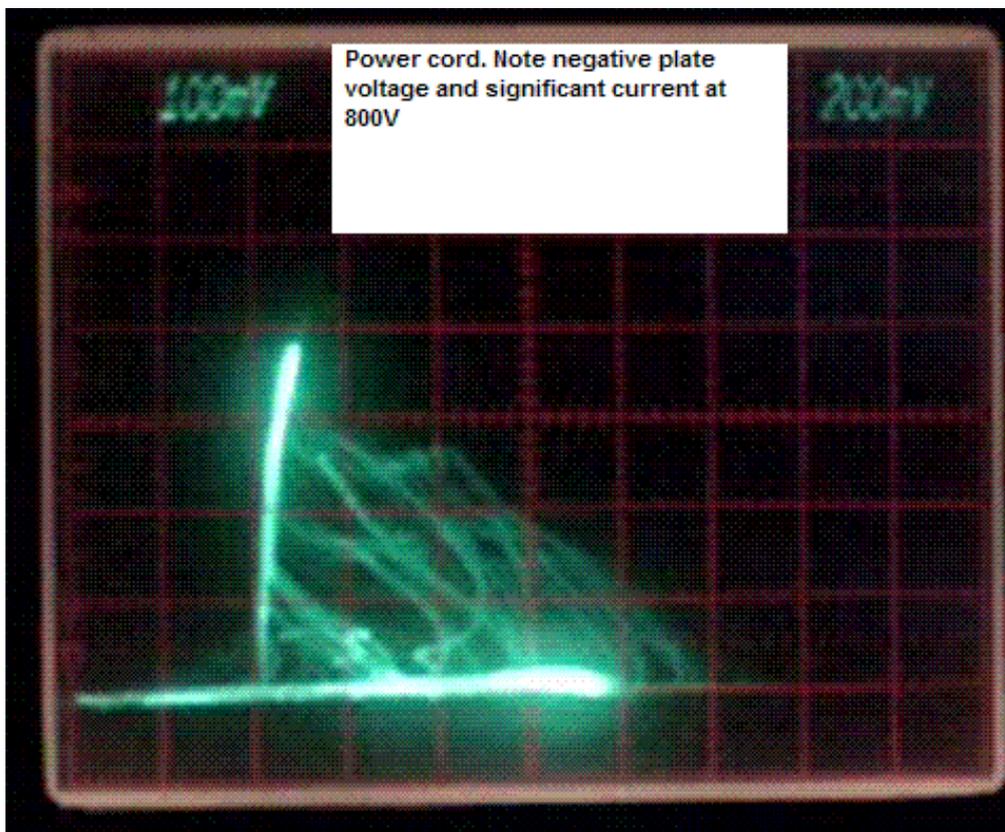

If used, RC conjunctive filters would influence the actual plate voltages experienced, and MOVs would start to influence plate voltages whenever the MOV voltage reached its clamping level.


Open-circuit output assessment

A 100W amp with quad 6L6GC PP output stage was used for testing the effect of an open-circuit output condition on generating over-voltage transients on the OPT primary windings.

The test applied 2 sinewave cycles of 30Hz to the amp input, and a high preamp gain effectively drove the fixed-bias PP output stage with a high magnitude square wave. For one side of the PP output stage, the waveforms of plate voltage and cathode current (of one 6L6GC) were acquired as shown below.

The plots show the plate voltage (orange trace 220V/div) and cathode current (blue trace 100mA/div) waveforms for the 2-cycle burst. The B+ was 500V, and idle cathode current was 25mA (per tube), as identified by the left-hand side initial values in the 2 top plots (relative to the left hand axis markers showing 0V and 0mA at 2 divs up). The overload conditions forced a short voltage transient on the plate voltage at each input squarewave edge. For the drive signal edge where cathode current steps to zero, the plate voltage is pushed high and can clearly exceed 1kV (2x B+). At the time of the drive signal edge when the cathode current of the other side of the PP stage steps to zero, the plate voltage in the plot is forced by transformer action to below 0V for a short transient.

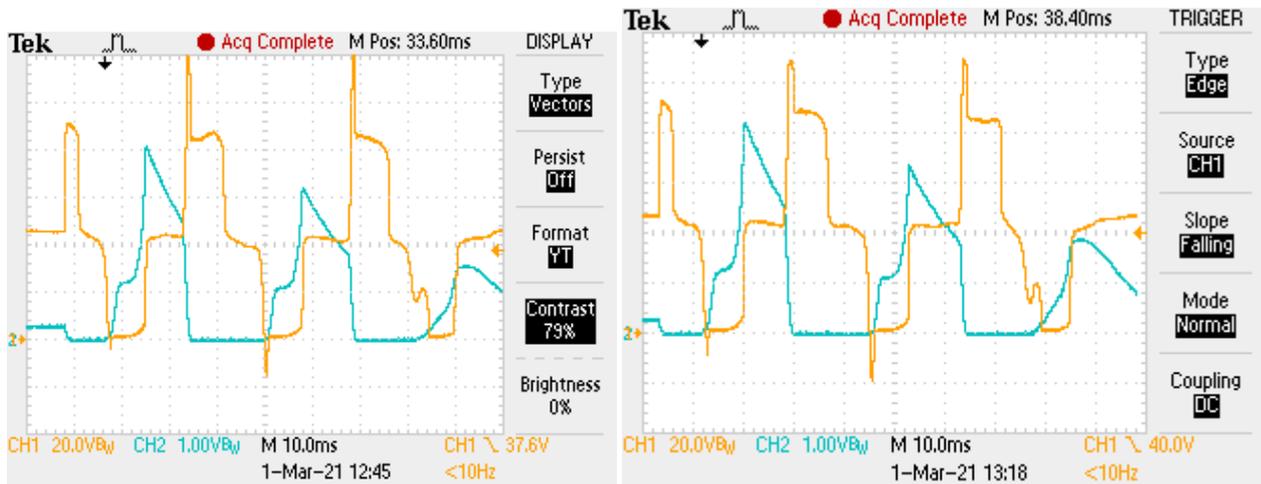
The right hand side plot shows about the same operating conditions as the left side plot, but with a MOV across each half-primary winding. Each MOV had a 612Vdc min 1mA rating, and the plot on the right shows the MOV restricting the plate voltage to about 1150V (650V above B+). If the overdrive conditions were increased, the transient voltage below 0V would also have been noticeably clipped.



No MOVs

With MOVs

With respect to the B+ level of +500V, the unclipped positive going transient has a higher magnitude than the negative going transient. That difference is likely due (in part) to the positive going transient being caused by the self-inductance of that half-winding, whereas the negative going transient would be caused by the inductance of the other half-winding transforming its voltage over to the probed half-winding. The capacitance of that anode junction to ground, and to B+, plays a significant part in absorbing the inductive energy, and there is also some leakage inductance energy that just transfers to the positive going transient in the plot.

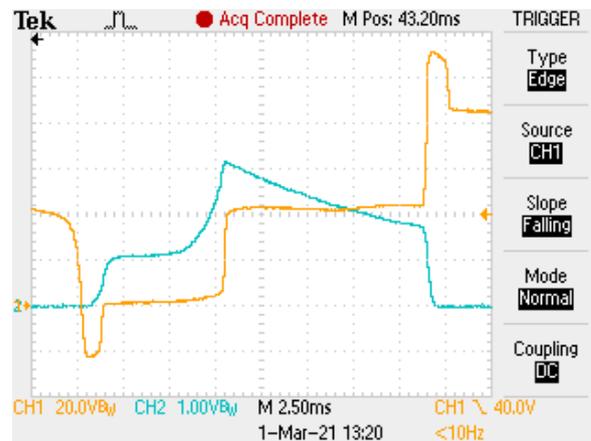

The time expanded plot above shows the clipped voltage waveform in more detail for when both positive and negative transients are constrained by the one MOV across the half-primary winding. The voltage rise during MOV conduction in the plot is about 50V, which for the CNR 10D681K MOV used indicates a peak MOV current of about 2-3mA (ie. a minimum dynamic damping resistance of about 200kΩ) for about 1ms, and an average power dissipation of nearly 750Vx3mA x 1ms / 16.6ms = 0.13W (ie. <0.4W for indefinite life).

Testing for a failed OT

The best first check to do on a suspect OT is to measure the OT's primary and secondary winding resistances using an ohmmeter (resistance range on a multimeter). The primary winding(s) resistance should easily show up on a meter as tens or hundreds of ohm, depending on the power rating of the OT, and is easily measured when the amplifier is off (pulling the output tube or tubes should disconnect all circuitry from an OT's plate terminal, but reference to a circuit schematic is worthwhile). The half-primary windings on a PP OT (CT to each plate terminal) should have similar resistance, but are unlikely to be exactly the same (especially for lower quality PA OT's). The OT secondary windings are likely to measure very low in resistance (disconnect the speaker first), and it may be difficult to determine a winding's resistance as it can measure like a short circuit. Connecting the meter probes together can give a zero or close to zero reading, and then measuring the winding resistance may show a slightly higher reading. A high or over-range resistance would likely indicate an open-circuited winding fault.

If there is no obvious winding resistance concern, then the next step is more complicated, and would involve applying say 5VAC to 12VAC (eg. from a power transformer secondary) to the primary winding (or PP half winding), and then measuring the AC voltage on the secondary windings (and on the other half-primary winding). Knowledge of the OT winding impedances can be used to determine the turns ratio's between the primary and secondary windings, and hence the turns ratio and the applied signal voltage can indicate the level of secondary voltage that should be measured. [Output transformer MS Excel calculation spreadsheet](#)

If a reasonable voltage level is not measured across a winding or windings, then there may be an internal short type fault between some turns within one of the windings (ie. an internal short circuit between two adjacent turns within a winding will exhibit a normal winding resistance, but would cause the transformer to lose its voltage transfer ratios between windings on the same core).

Another worthwhile test to perform is to measure the insulation resistance between primary windings and the core, and between the primary windings and the secondary (speaker) windings. This test is done with a megohm meter at a hazardous voltage so is a safety risk. A typical megohm test voltage is 1kVDC, which almost any OT can sustain between primary windings and core or secondaries, and the measured resistance should typically be well above 20 M Ω . Breakdown of insulation in the transformer can occur as primary winding voltages reach transiently high levels.

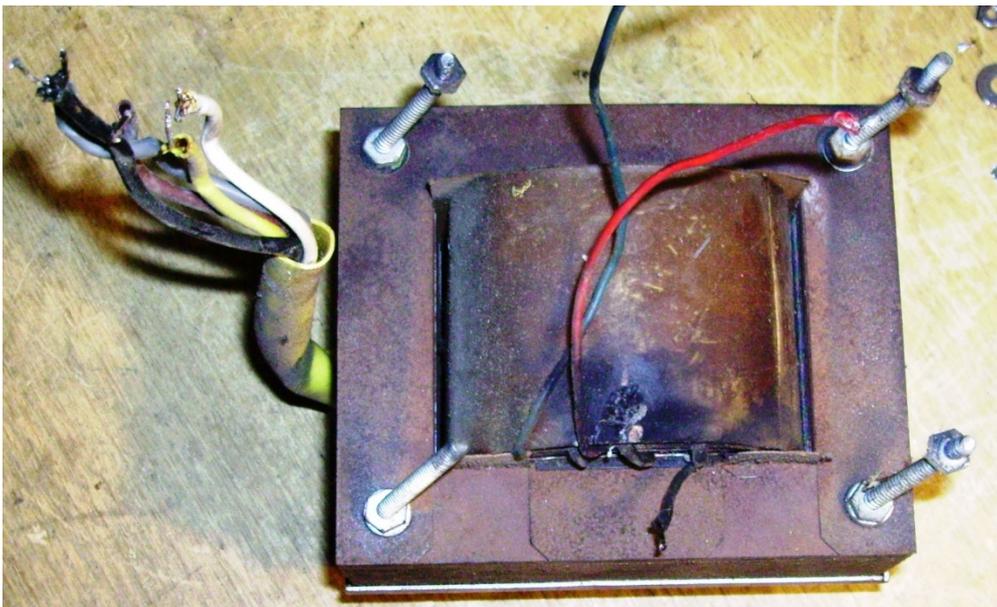


Figure 10. A dropped amplifier caused this OT to bend its mounting bolts and short a primary plate wire to chassis – no internal wiring damage, so it's back in the amp and working now.

A more pernicious fault to identify is if some internal arcing between turns or winding layers occurs only during operation at the on-set of high signal level conditions, where the speaker output level may quickly fall away. This type of fault usually continues to degrade internal insulation, and so the symptoms get worse. Testing for this type of fault may be difficult, and require continued operation in the amplifier, but with protections in place if a hard fault occurs. There are also a variety of relatively simple test techniques for detecting shorted turns – [one such technique](#). If an OT has failed, then other related parts need to be checked for stress or failure – especially output stage valves, and screen stopper resistors.

Note that symptoms of no 'speaker output' may not be due to the OT even though everything else appears initially to be ok, as highlighted by the discussion in gretschpages.com/forum/ by mrock. And some OT faults may appear to be unfixable, but end up being quite easy to fix as the fault is not internal to windings.

The charred pin 7 socket terminal for a 6BW6 anode (novel 6V6) highlights a need for careful inspection to show up arcing.

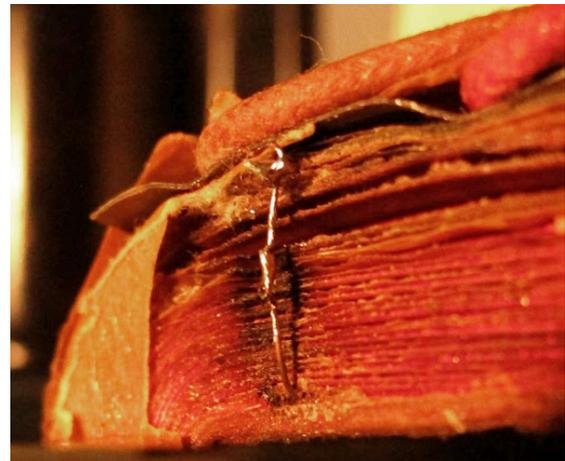


Figure 11. Repairable fault in output transformer.

Figure 11 shows a repairable fault in an OT. Arcing from half-primary winding layer edge turns to the other half-winding plate link wire had caused an obvious area of over-heating damage that resulted in an open-circuit. The OT was repaired by replacing the link wire, and carefully insulating it (not shown). [[Hoffman Amplifiers Forum](#) but thread now lost]. Figure 12 shows a lucky primary winding repair – with broken turns in outer layer on the edge – made somewhat difficult due to beeswax potting.

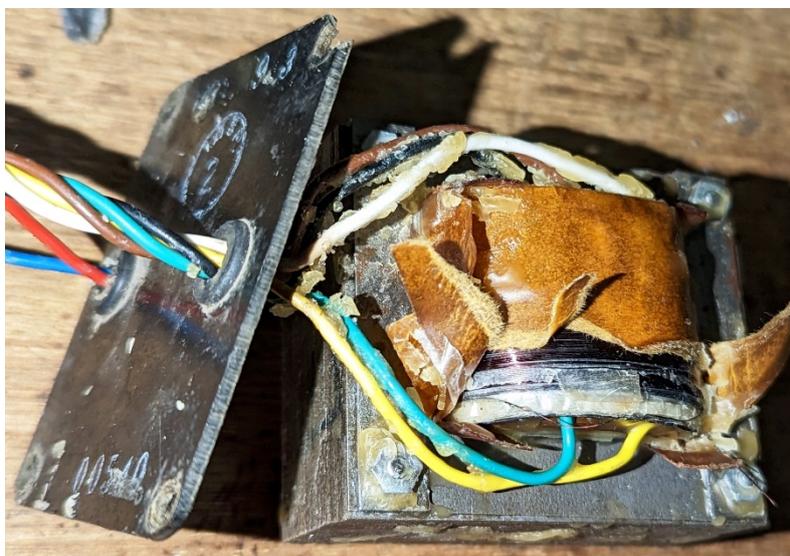


Figure 12. Broken turns repaired in outer primary winding of 3W SE A&R OT933.

Power transformer and choke protection

Similar to an output transformer, the power transformer (PT) in a valve amplifier, and the choke in a choke input filter, can also be subject to over-voltage and over-current stresses. Over-voltage transients can stress insulation within the PT and choke windings as well as parts connected to the windings, such as the primary side AC switch, any secondary side fuses, standby switches and diodes. Parts in the power supply and amplifier output stage can fail and cause over-current stress within the PT and choke.

Over-voltage protection

When the amplifier power switch is turned off, the PT winding currents are stopped abruptly, which could exacerbate arcing on the mains switch's contact, leading to increased pitting of the switch contact. This is not such an issue if the PT winding currents are low – such as when the amp is in standby or idling, and if the switch off occurs at the time in the mains cycle where current is not passing through a rectifier diode. A MOV with a suitable voltage rating on the primary side winding, and even MOV's on secondary side windings could be used to reduce over-voltage transients generated on those windings.

Some amps use a standby switch that opens the PT secondary CT connection to 0V, which could interrupt a large current level through one of the secondary HT windings, especially if the standby switch is toggled a few times and the main filter caps are being charged up under full idle load conditions. The leakage inductance in that winding can stress the standby switch, as well as the diodes, and a MOV across each secondary HT winding could be appropriate.

Often a power supply choke has a sizeable filter capacitor on each end of the choke, as in a CLC type filter, where the capacitors dampen any possibility of a transient voltage across the choke due to a fault that abruptly stops choke current. However, if just a choke input filter is used after the rectifier diodes, then a fault (or even during regular operation) could generate a high voltage at the diode-choke node as there is little stray node capacitance to dampen the voltage at that end of the choke. GEC recommended an RC snubber across the choke [[An approach to audio frequency amplifier design, GEC, 1957](#)]. Some designs add a small capacitance to ground at that node for noise filtering, where for a 10H choke dumping 0.2J (from 200mA current step) into a 100nF capacitor, the voltage on that cap could change by 2kV as $\frac{1}{2}LI^2$ transfers to $\frac{1}{2}CV^2$. Some designs add an RC zobel network across the choke to improve the filtering response of the choke (resonant frequency of parallel choke L and zobel C set at ripple frequency so that impedance of "choke" to ripple is higher), and that 'ripple trap' network can certainly alleviate transient voltages. If a MOV (or zobel network) is added in parallel to the choke then its DC voltage rating needs to accommodate the turn-on condition where one end of the choke is at $+VAC_{pk}$ and the other end is still at 0V, and similarly where one end of the choke is at $-VAC_{pk}$, and other end is at peak B+ (ie. $+VAC_{pk}$), which is more onerous. So a DC voltage rating of at least $2 VAC_{pk}$ is needed for parts across the choke. Parts from the diode-choke node to ground need a DC voltage rating of at least VAC_{pk} . Those situations are likely to require a series connection of MOVs, and any capacitor is likely to be a physically large metalized plastic type. The resistor in the zobel network is mainly to dampen the resonant Q of the LC, along with choke ESR. Any capacitor used in these locations should be carefully rated for continuous VAC operation, and preferably have an X type rating for failure protection.

Covering a MOV or in-rush limiting thermistor placed on a mains primary side, with a sleeve of heatshrink tubing is a good idea so as to constrain the part if it becomes damaged.

Over-current due to failed valve diodes

Adding a silicon diode (one or more 1N4007 in series depending on the HT level – see '[Power supply issues for tube amps](#)') in series with each anode of a diode valve (as shown in Figure 4) can avoid shorting out the power transformer HT secondary winding if the valve diode starts to conduct continuously, or arcs between anode and cathode (eg. gassy tube). When using protection solid-state diodes, a valve diode fault could go unnoticed, unless it is observed as an increase in hum, or as a B+ level when B+ AC and DC voltage is next checked, in which case it should be fixed as soon as possible. Using an insulation resistance tester at 1kVdc is also a [practical maintenance action](#) to check for valve diode performance.

Rectifier valves with a 6.3V heater (eg. 6V4/EZ80, 6X4, 6X5, 6CA4/EZ81) are typically powered from a dalmura.com.au/projects/

secondary winding with CT connected to ground, and as the valve ages the cathode-to-filament interface can become a low resistance or short, which then loads or short-circuits the high voltage secondary winding. This type of fault can be alleviated by disconnecting the heater winding CT, and using a fixed or tuned heater humdinger (as used for [hum reduction](#)) connection to ground which should then fail open, or alternatively [fusing the high-voltage CT](#).

Over-current due to failed parts

Parts within a valve amplifier age, and can fail causing a high current to be drawn from the PT. Any series resistance in the circuit loop between the PT, the failed part, and ground, in which the fault current flows will suppress the prospective fault current level (ie. the maximum level that the fault current could reach).

A failed part like the first main filter capacitor may only have the PT winding resistance and diode resistance to constrain the fault current. A failed part like an output stage valve will typically have a higher fault circuit resistance (due to output transformer primary winding resistance and maybe a valve cathode resistor) and hence the prospective fault current level will be lower. Any fuse used to interrupt such a fault current has to be able to pass the normal operating current of the circuit, but also open in an acceptably short time should a fault occur, so that the PT winding is not damaged. See [Valve Amp Fusing](#).

A power supply with a valve diode rectifier can be particularly prone to diode arcing, which effectively short-circuits the secondary HT winding [see [Power Supply Issues for Valve amplifiers](#), section 7.3] and is not protected by a fuse located in the CT link of the secondary winding to ground. Arcing can arise from valve aging where internal gas conduction or leakage across insulating surfaces or loose materials cause an arc to occur between the cathode and the negatively biased anode. Arcing can also arise from an excessively high current during power-on, when the cathode has not yet developed a sufficient electron cloud to support the demanded current [see [Tomer 1960](#), p.18-19]. The modern-day mitigation method for those failure causes is to insert a solid-state diode (with sufficient PIV rating) in series with each anode of a valve rectifier [see [Power Supply Issues for Valve amplifiers](#), section 2].

A power supply with a valve diode rectifier that shares its AC heater with other valves in an amplifier can be prone to cathode-heater short-circuit failure (eg. for 6.3V rectifier valves like 6V4, 6X4, 6X5, 6AU4, 6CA4). Aging may cause metal migration and spurs through the heater insulation coating, which may sustain a continuous current from B+ to the ground path through the 6V heater. This type of fault may be alleviated by a fuse on the PT secondary winding, especially if the heater winding has a CT tap that is grounded - but fuse protection performance could be strongly influenced by any hum reduction parts (if used) such as humdinger resistors or pot, or an elevated heater configuration, as they could suppress the fault current to a level where the fuse may not operate. One form of fault alleviation may be to use hum reduction parts that fail before the power transformer secondary winding over-heats, such as to use lower powered humdinger resistors, or trimpot, although that may cause collateral damage to other valves whose heaters may acquire a dc voltage that rises above their ratings (see overcurrent section).