

Separate amplifier and power-supply chassis reduce hum, allow uncluttered layouts.

Easily-built

American versions of
the Williamson circuits

give superb results

at comparatively

low cost

PRACTICAL WILLIAMSON AMPLIFIER

By FRANCIS A. GICCA

FOR many years the high-fidelity fan has been looking for the "perfect" amplifier circuit, one that would be flat throughout the audio range, practically distortionless, with adequate power output, and relatively inexpensive. Many circuits have been devised and many have come close to the ideal, but each has left something to be desired. The most popular circuit of recent years is the Williamson amplifier.

Although the original specifications called for the use of a British-made output transformer (Partridge) and British tube types (KT-66), several American versions have appeared. Complete Williamson amplifier kits, including punched chassis, are now available from several American manufacturers, including Heathkit, Stancor, and UTC. Other American companies, such as Acrosound, ADC, Peerless, and Triad, are producing special Williamson output transformers. Many distributors are also supplying complete or foundation kits. This amplifier used Stancor transformers and follows that company's version of the Williamson circuit. (See Figs. 1 and 2.)

Construction

The power supply is built on a separate chassis to keep a.c. transformer fields away from the amplifier. Power

is brought to the amplifier through a 4-wire cable.

Stancor suggests using two 9 x 7 x 2-inch chassis for the amplifier and power supply. However, this was found to be too small for the layout and wiring desired. We found an 11 x 7 x 2-inch aluminum chassis adequate.

The power supply itself is conventional and should cause no trouble. The core of the choke should be perpendicular to the core of the power transformer to reduce the effects of stray magnetic fields.

The layout of the amplifier is not critical, because of the isolated power supply. Be sure the 807's have enough ventilation. The layout used gave no trouble; it is suggested for ease of wiring.

The heater circuits should be wired first with twisted pair. These leads should run first to the 807's and then to the 6SN7's. To prevent ground loops all ground returns should be connected to a floating bus and the bus grounded to the chassis only at the input connector. Be sure to use insulated mountings for metal-shell decoupling capacitors and connect their negative terminals to the ground bus. Use insulated mountings also for the jacks in the cathode circuits of the 807's.

All resistors should have a tolerance of 10% or better. It is very important

that the starred resistors be matched pairs. If unbalance occurs in the direct-coupled stage it might bias the tube almost to cut-off. Unbalance in the phase-inverter circuit will cause unequal drive to the 807's. To get matched pairs take an ohmmeter to your parts distributor and measure resistors until you find two that give the same reading within 10% of the required value. Most distributors will let you do this. It is unnecessary to use a Wheatstone bridge to get two perfectly matched resistors; the ohmmeter will suffice.

A few precautions must be taken to prevent attenuation of the high audio frequencies. Do not use any shielded wire; mount all parts as far above the chassis as possible; keep all leads short; avoid cabling wires together; keep your wiring compact. It is amazing how much difference these small details can make. In this amplifier raising parts above the chassis extended the response 3 kc at the high-frequency end.

Tests and adjustments

Having completed the amplifier we started making the usual voltage checks. Suddenly we noticed one 807 glowing bright red just as the fuse blew out. We checked the setting of the potentiometer which balances the plate currents of the 807's. It was set at one

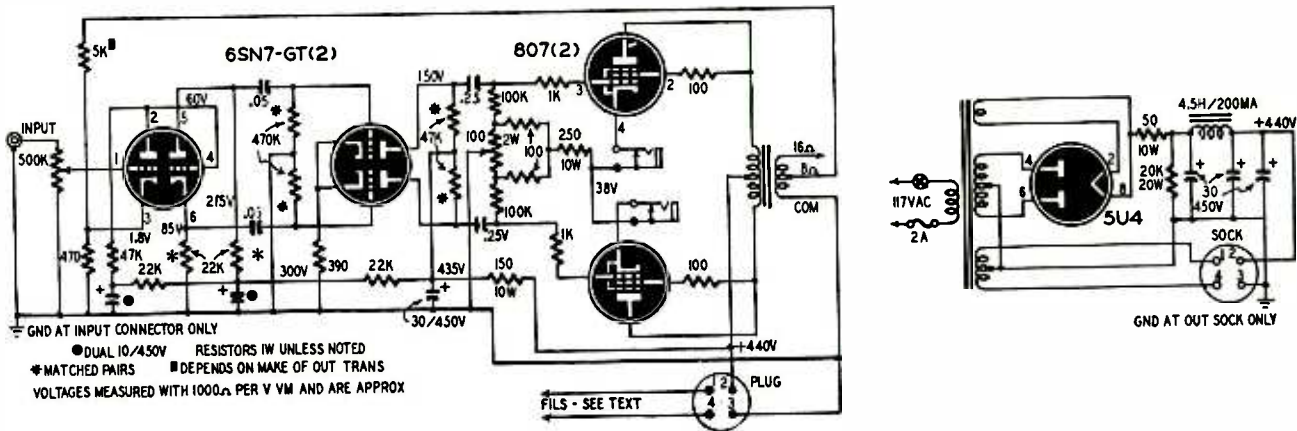


Fig. 1 (above)—The Stancor version of the Williamson amplifier circuit. Principal differences are the use of 807's instead of British KT66's, and R-C power-supply filtering in the first two stages. Fig. 2 (upper right)—The Stancor power supply schematic. Fig. 3 (right)—Schematic of the Heathkit model WA-P1 preamplifier-equalizer kit. The turnover switch compensates for the different frequency characteristics used in 78-r.p.m. and LP recordings. Bass and treble controls give flat response in midpositions, 15 db boost or cut at opposite ends. 12AY7 is a low-microphonic type.

end, so we reset it near the middle of its range and replaced the fuse. Again the 807 began to glow and the balancing control had no effect at all. We then checked the plate current of each tube and found one drawing 146 ma and the other drawing 23 ma. By this time we were worried. Tearing apart the balancing network we found nothing visibly wrong, so we suspected a faulty potentiometer and replaced it. Still the 807 glowed. In disgust we put in two new tubes and started over. Now everything was fine. The circuit balanced and both 807's drew normal current. We felt slightly silly when we found that one 807 was gassy. So—if your circuit does not balance—check the 807's first.

To balance the circuit plug a milliammeter into each of the jacks in turn and adjust the balancing potentiometer until both readings are equal at approximately 100 ma.

If the amplifier squeals, reverse the plate leads to the output transformer. This should correct the fault.

The response of the amplifier was checked with a Hewlett-Packard audio oscillator, an RCA audio voltmeter, and a Hewlett-Packard distortion analyzer. The frequency response is superior to broadcast standards and is truly high-fidelity. The unit has been in constant use for over four months and has

not developed any trouble. It is currently being used as a standard for free-field acoustical measurements. The unit is free from any inherent circuit noise or microphonics and is very stable. It is well worth the time and trouble put into its construction.

(A preamplifier and equalizer should be used with this amplifier to obtain full output and optimum performance when using low-output pickups such as the variable reluctance and some magnetic types. A number of preamplifier-equalizer circuits have been developed by manufacturers and distributors of high-fidelity amplifiers. Some of these include loudness controls and rather elaborate preset equalizer circuits for almost every type of recording characteristic. Others are simpler but equally effective for most applications.

Typical of the simpler circuits is the Heathkit WA-P1 preamplifier-equalizer shown in Fig. 3. A switch selects either of two low-gain inputs for crystal pick-up or tuner, or the high-gain channel for magnetic pickups. A two-position turnover switch in the latter channel has positions for 78-r.p.m. and LP recordings. Separate bass and treble controls provide up to 15 db boost or cut at 20 and 20,000 cycles, respectively. Signal voltage input required to develop 1.2 volts output—the approximate value required

to drive the amplifier to full output—is 0.2 volt into the low-gain channels and .004 volt for the high-gain input circuit.—Editor)

Materials for Williamson amplifier

Resistors: 2—470,000 ohms, (matched), 2—100,000 ohms, 1—47,000 ohms, 2—22,000 ohms, 2—22,000 ohms (matched), 1—5,000 ohms, 2—1,000 ohms, 1—470 ohms, 1—390 ohms, 4—100 ohms, 1 watt, 10%; 2—47,000 ohms (matched), 2 watt, 10%; 1—250 ohms, 1—150 ohms, 1—50 ohms, 10 watt, wire-wound; 1—20,000 ohms, 20 watt, wire-wound; 1—500,000-ohm potentiometer, audio taper; 1—100-ohm potentiometer, 2 watts.

Capacitors: (Paper) 2—.25 μ f, 2—.05 μ f, 600 volts. (Electrolytic) 3—30 μ f, 475 volts; 1—30 μ f, 2—10 μ f, 450 volts.

Transformers: 1 Williamson output transformer (Stancor No. A-8054 or equivalent); 1 power transformer; (Stancor PC-8412 or equivalent); 1 filter choke (Stancor C-1411 or equivalent).

Miscellaneous: Tubes: 2—6SN7-GT; 2—807; 1—5U4-G. 2 chassis, 11 x 7 x 2 inches; 3 octal sockets; 2—5-prong sockets; 2—4-prong sockets; 2—4-prong plugs; 1—input connector; 2 circuit-opening jacks; 2 insulated plate-cap connectors; 1 output terminal strip; 1 fuse holder; 1—2-amp fuse; 1 s.p.s.t. toggle switch; 1 line cord and plug; wire, solder, terminals, hardware.

Materials for Preamplifier

Resistors: 1—10 megohm; 6—100,000 ohms; 3—22,000 ohms; 1—3,300 ohms; 2—2,200 ohms, 1/2 watt; 1—10,000 ohms, 1 watt. 3—1-megohm potentiometers.

Capacitors: (Paper) 4—.002 μ f; 2—.02 μ f; 5—.05 μ f, 600 volts; (Mica or ceramic) 1—200 μ f; (Electrolytic) 2—20 μ f, 350 volts; 1—20 μ f, 25 volts.

Miscellaneous: 1—12AX7 or 12AY7 tube; 1—12AU7 tube; 2—9-pin miniature tube sockets; chassis, switches, hardware.

—end—